


Contents

Question 1.	2
Question 2.	3
Question 3.	4
Question 4. Sketch the hardware each circuit implies	5

Collaborators: Cameron Jennings

Question 1.

 - (a) Draw out the state diagram of this circuit. Don't forget a reset state.



- (b) Implement modules `hw1p1` and `hw1p1_tb`, which thoroughly simulates an instance of called dut.

Implemented in SystemVerilog, submitted on gradescope


Question 2.



- (a) Implement modules `hw1p2` and `hw1p2_tb` which thoroughly simulates an instance of `hw1p2` called `dut`.

Implemented in SystemVerilog


Question 3.

(a) Draw out the state diagram for the FSM

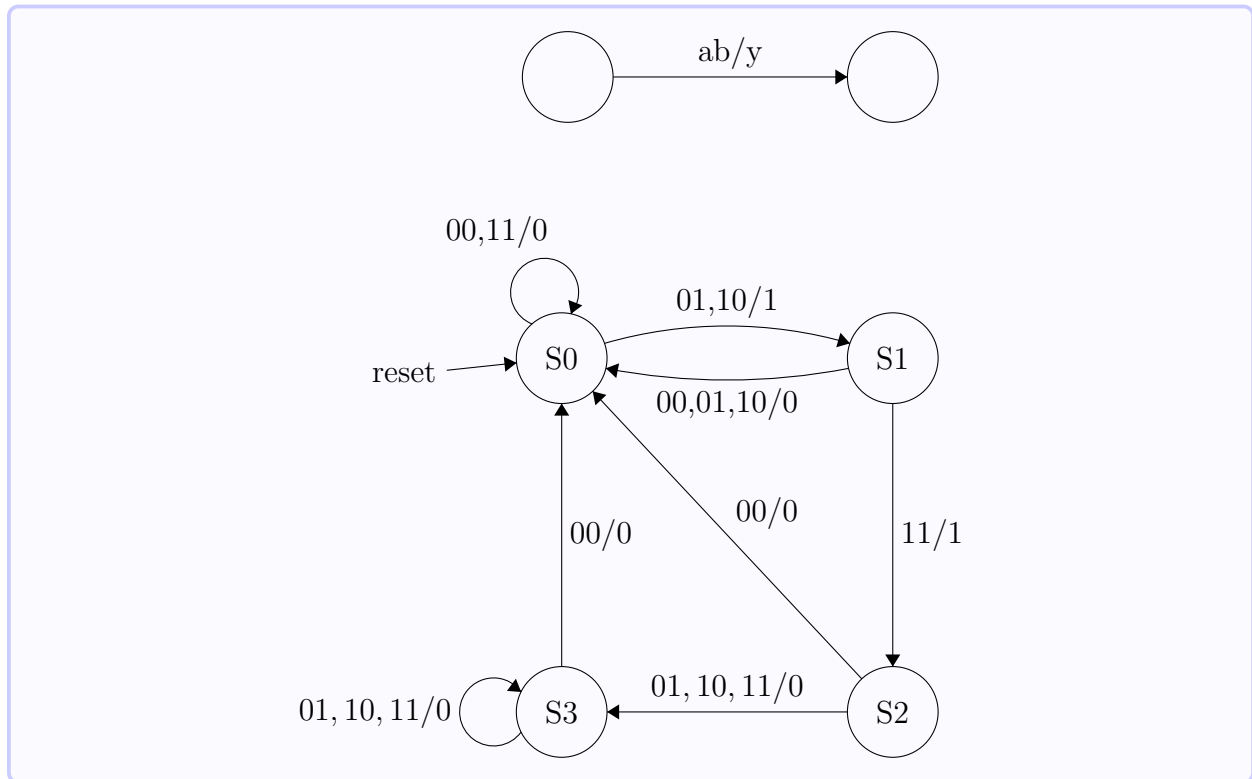

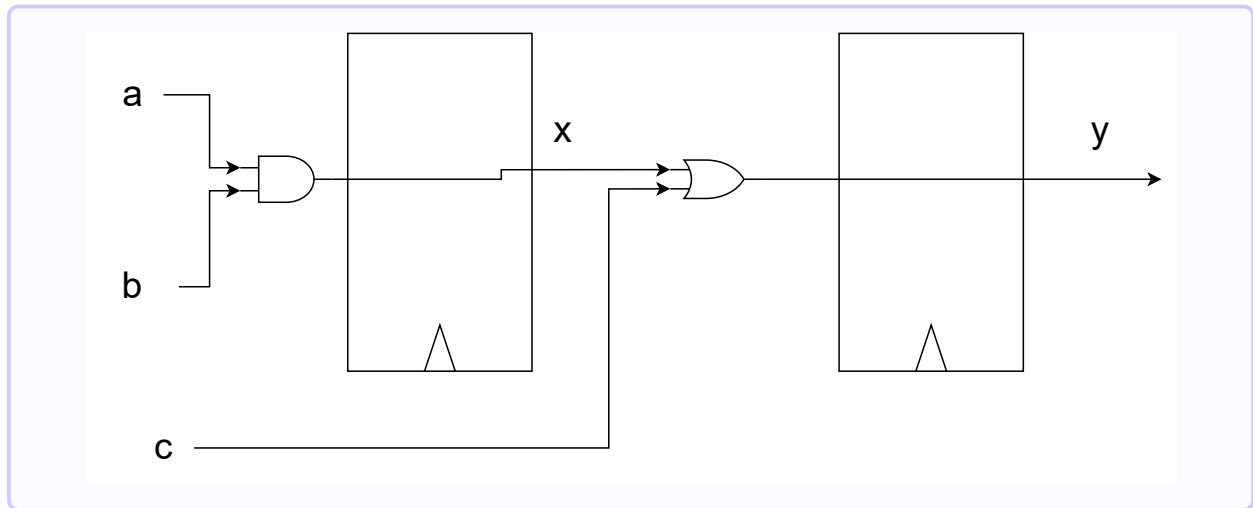 Question 4. Sketch the hardware each circuit implies**(a) Circuit 1 Parallel****(b) Circuit 1 Sequential**

(c) Circuit 2 Parallel

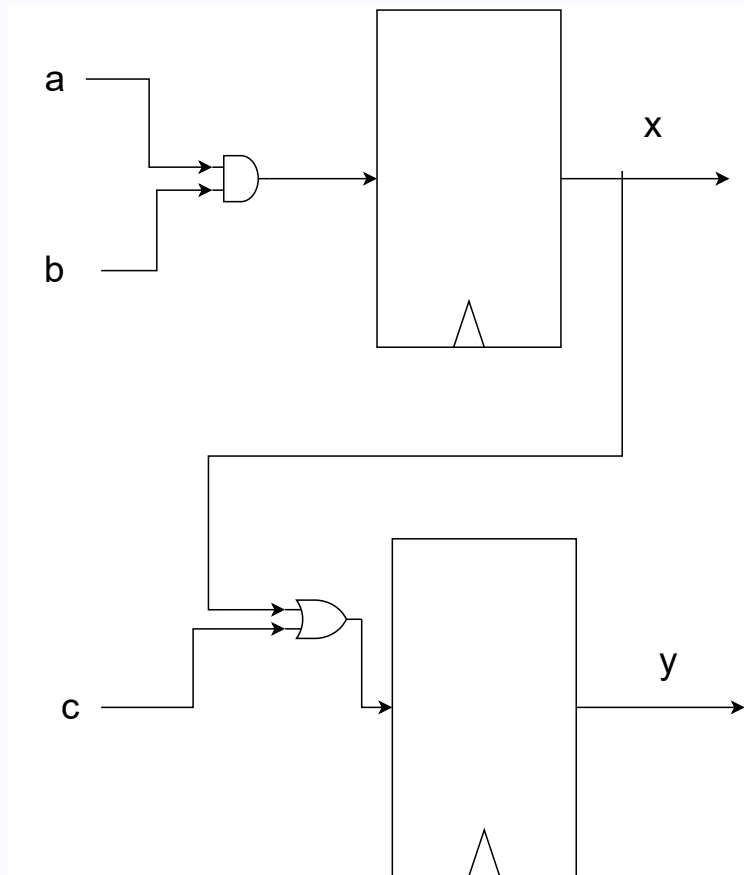

(d) Circuit 2 Sequential