

EE/CSE 371
Design of Digital Circuits and Systems


Lecture 7: ASM with Datapath II

SDS

Synchronous Digital System.


Triggering
ACTIONS
in datapath

External
inputs

 

Control
Signal

Status
Signal

 

Data
in

Data
out

CLK

Status
indicators


DECISIONS
made in Controller

ASMD Design Procedure

- ❖ From problem description or algorithm pseudocode:
 - 1) Identify necessary datapath components and operations**
 - 2) Identify states and signals that cause state transitions**
(external inputs and status signals), based on the necessary sequencing of operations
 - 3) Name the control signals** that are generated by the controller that cause the **indicated operations** in the datapath unit
 - 4) Form an ASM chart for your controller**, using states, decision boxes, and signals determined above
 - 5) Add the datapath RTL operations** associated with each control signal

Design Example #1

❖ System specification:

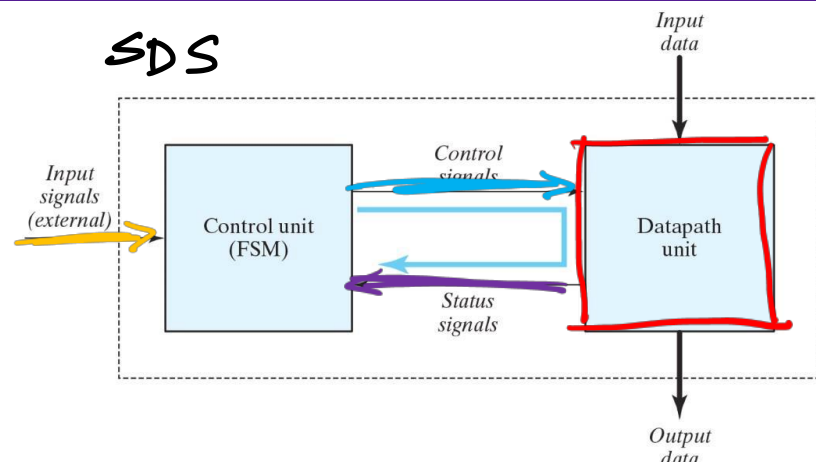

datapath ■ Flip-flops E and F

datapath ■ 4-bit binary counter A = 0bA₃A₂A₁A₀

inputs to control ■ Active-low reset signal reset_b puts us in state S_idle, where we remain while signal Start = 0

control signals ■ Start = 1 initiates the system's operation by clearing A and F. At each subsequent clock pulse, the counter is incremented by 1 until the operations stop. ↑ clr_A-F

status signals ■ Bits A₂ and A₃ determine the sequence of operations: ↑ incr_A


• If A₂ = 0, set E to 0 and the count continues ← clr_E

• If A₂ = 1, set E to 1; additionally, if A₃ = 0, the count continues, otherwise, wait one clock pulse to set F to 1 and stop counting (i.e., back to S_idle) ← set_F

control signals

Design Example #1


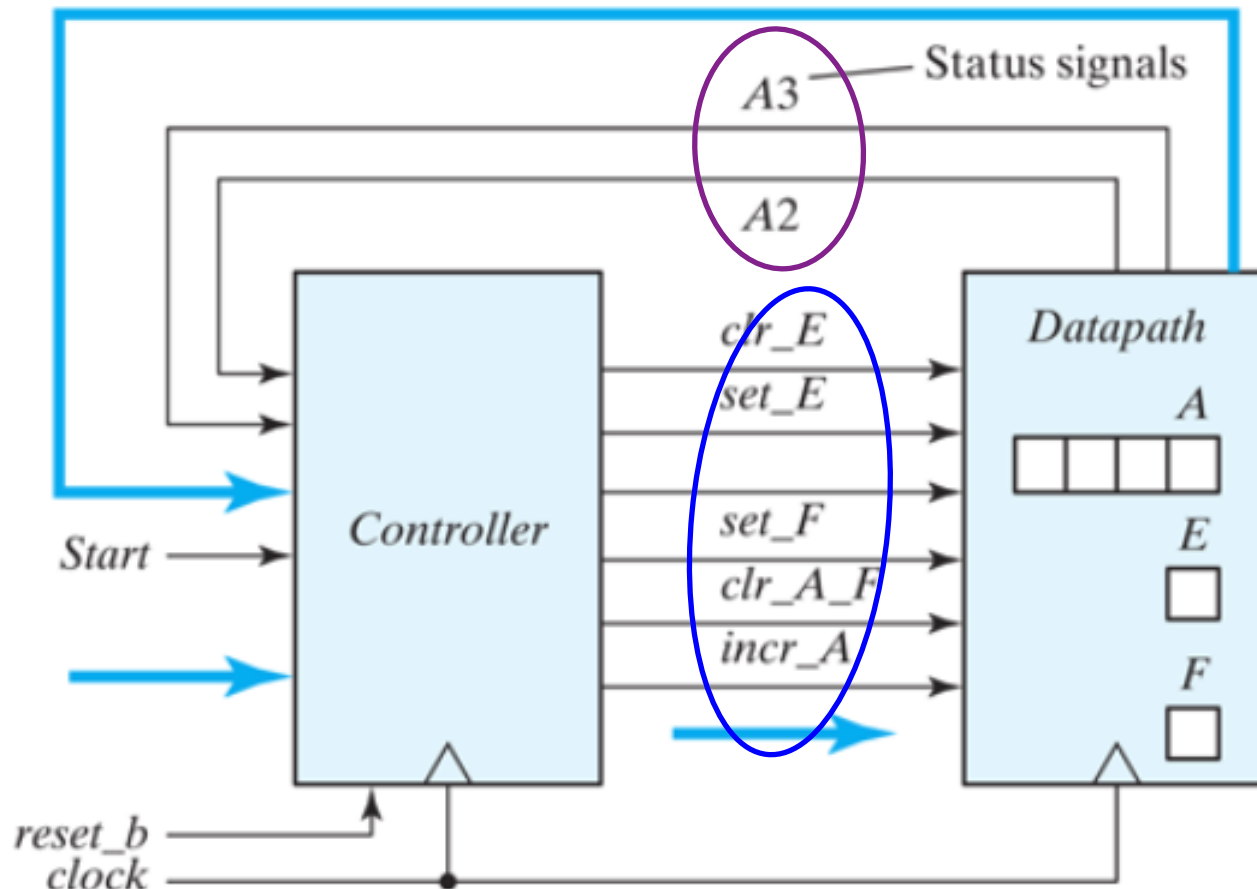
- ❖ The system can be represented by the following block diagram:



Design Example #1 (ASM \rightarrow ASMD Chart)

- ❖ Synchronous or asynchronous reset?

  for synchronous reset, add decision box on reset-b out of every state box:



Design Example #1 (Timing)

❖ Sequence of operations:

Time ↓

Counter				Flip-Flops		Conditions	State
A_3	A_2	A_1	A_0	E	F		
X	X	X	X	1	X	<u>Start</u>	S_idle
0	0	0	0	1	0	$A_2 = 0, A_3 = 0$	S_count
0	0	0	1	0	0		
0	0	1	0	0	0		
0	0	1	1	0	0		
0	1	0	0	0	0	$A_2 = 1, A_3 = 0$	
0	1	0	1	1	0		
0	1	1	0	1	0		
0	1	1	1	1	0		
1	0	0	0	1	0	$A_2 = 0, A_3 = 1$	
1	0	0	1	0	0		
1	0	1	0	0	0		
1	0	1	1	0	0		
1	1	0	0	0	0	$A_2 = 1, A_3 = 1$	
1	1	0	1	1	0		S_F
1	1	0	1	1	1		S_idle

Handwritten annotations:

- clr_A_F (red arrow) points to the first row (X, X, X, X).
- clr_E (red arrow) points to the second row (0, 0, 0, 0).
- set_E (red arrow) points to the sixth row (0, 1, 0, 0).

Design Example #1 (Logic)

❖ Controller:

■ State Table:

$S_idle = \overline{P_1} \cdot \overline{P_0}$
 $S_count = \overline{P_1} \cdot P_0$
 $S_F = P_1 \cdot P_0$

Present-State Symbol	Present State		Inputs			Next State		Outputs				
	P_1	P_0	Start	A_2	A_3	N_1	N_0	set_E	clr_E	set_F	clr_A_F	incr_A
S_idle	0	0	0	X	X	0	0	0	0	0	0	0
S_idle	0	0	1	X	X	0	1	0	0	0	1	0
S_count	0	1	X	0	X	0	1	0	1	0	0	1
S_count	0	1	X	1	0	0	1	1	0	0	0	1
S_count	0	1	X	1	1	1	1	1	0	0	0	1
S_F	1	1	X	X	X	0	0	0	0	1	0	0

■ Logic:

$$N_1 = (PS == S_idle) \& A_2 \& A_3$$
$$N_0 =$$
$$set_E =$$
$$clr_E = (PS == S_idle) \cdot \overline{A_2}$$

$$\checkmark set_F =$$
$$\checkmark clr_A_F =$$
$$\checkmark incr_A =$$

Design Example #1 (SV, Controller)

control signals (out)
status signals (in)
external inputs (in)

```
module controller (set_E, clr_E, set_F, clr_A_F,  
                  incr_A, A2, A3, Start, clk,  
                  reset_b);
```

// port definitions

```
input logic Start, clk, reset_b, A2, A3;  
output logic set_E, clr_E, set_F, clr_A_F, incr_A;
```

// define state names and variables

```
enum {S_idle, S_1, S_2 = 3} ps, ns;
```

// controller logic w/synchronous

```
always_ff @(posedge clk) asynchronous reset  
    if (~reset_b) negedge reset  
        ps <= S_idle;  
    else  
        ps <= ns;
```

// next state logic

```
always_comb
```

```
case (ps)
```

```
    S_idle: ns = Start ? S_1 : S_idle;
```

```
    S_1:     ns = (A2 & A3) ? S_2 : S_1;
```

```
    S_2:     ns = S_idle;
```

```
endcase
```

// output assignments

```
assign set_E = (ps == S_1) & A2;
```

```
assign clr_E = (ps == S_1) & ~A2;
```

```
assign set_F = (ps == S_2);
```

```
assign clr_A_F = (ps == S_idle) & Start;
```

```
assign incr_A = (ps == S_1);
```

```
endmodule // controller
```

Design Example #1 (SV, Datapath)

control signals (in)
 status signals (out)
 external inputs (in)
 external outputs (out)

```

module datapath (A, E, F, clk, set_E, clr_E, set_F, clr_A_F,
                 incr_A);

  // port definitions
  output logic [3:0] A;
  output logic E, F;
  input  logic clk, set_E, clr_E, set_F, clr_A_F, incr_A;

  // datapath logic
  always_ff @(posedge clk) begin
    if (clr_E)      E <= 1'b0;
    else if (set_E) E <= 1'b1;
    if (clr_A_F)
      begin
        A <= 4'b0;
        F <= 1'b0;
      end
    else if (set_F)  F <= 1'b1;
    else if (incr_A) A <= A + 4'h1;
  end // always_ff

endmodule // datapath
  
```


else if
to avoid
conflicts!

Design Example #1 (SV, Top-Level Design)

```
module top_level (A, E, F, clk, Start, reset_b);  
  
    // port definitions  
    output logic [3:0] A;  
    output logic E, F;  
    input logic clk, Start, reset_b;  
  
    // internal signals (control signals and status signals that aren't outputs)  
    logic set_E, clr_E, set_F, clr_A_F, incr_A;  
  
    // instantiate controller and datapath  
    controller c_unit (.set_E, .clr_E, .set_F,  
                      .clr_A_F, .incr_A, .A2(A[2]),  
                      .A3(A[3]), .Start, .clk,  
                      .reset_b);  
  
    datapath d_unit (.*);  
  
endmodule // top_level
```

Design Example #2: Fibonacci

 - ❖ Design a **sequential** Fibonacci number circuit with the following properties:



- **i** is the desired sequence number
- **f** is the computed Fibonacci number:

$$fib(i) = \begin{cases} 0, & i = 0 \\ 1, & i = 1 \\ fib(i-1) + fib(i-2), & i > 1 \end{cases}$$

<i>i</i>	<i>fib</i>
0	0
1	1
2	1
3	2
4	3
⋮	5
	8
	⋮

- **ready** means the circuit is idle and ready for new input
- **start** signals the beginning of a new computation
- **done_tick** is asserted for 1 cycle when the computation is complete

Design Example #2 (Pseudocode)

$i = 0$
 if ($i == 0$) return 0;
 $zero_f$
 $init$
 $fm1 = 1;$
 $fm2 = 0;$
 n_lt_i
 for n from 2 to $i-1$ (inclusive):
 $iterate$
 $temp = fm2;$
 $fm2 = fm1;$
 $fm1 = temp + fm2;$
 return $fm1 + fm2;$


Some Variants:

- could have explicitly shown $i == 1$ base case
- any loop bounds that execute $i-2$ times will work
- could have explicitly used a third $f = fm1 + fm2$ variable


❖ Pseudocode analysis:

- Variables are part of **datapath**; assignments become RTL operations
- Chunks of **related actions** should be triggered by **control signals**
- **Decision** points become **status signals**

Design Example #2 (Control-Datapath)

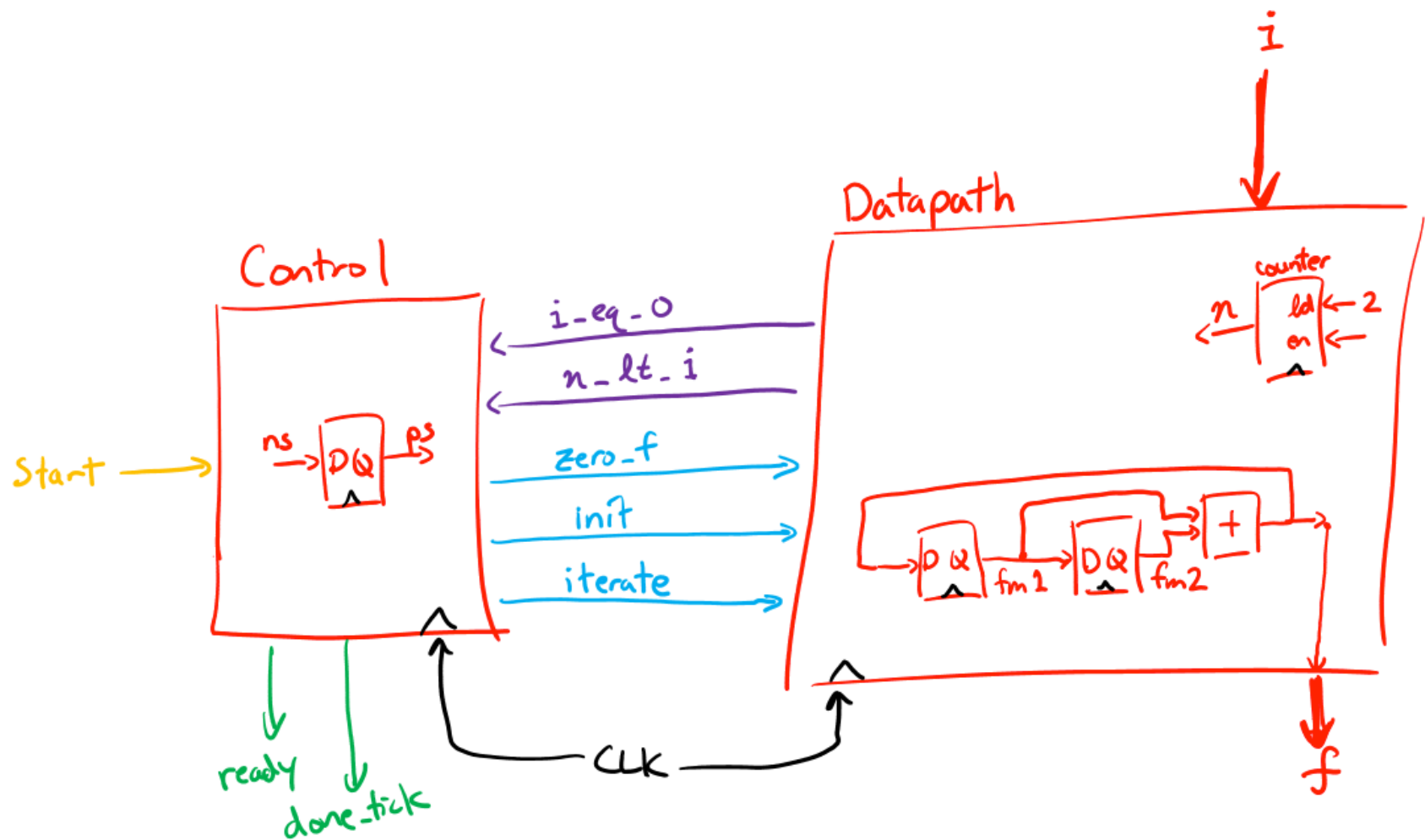

Design Example #2 (ASMD Chart)

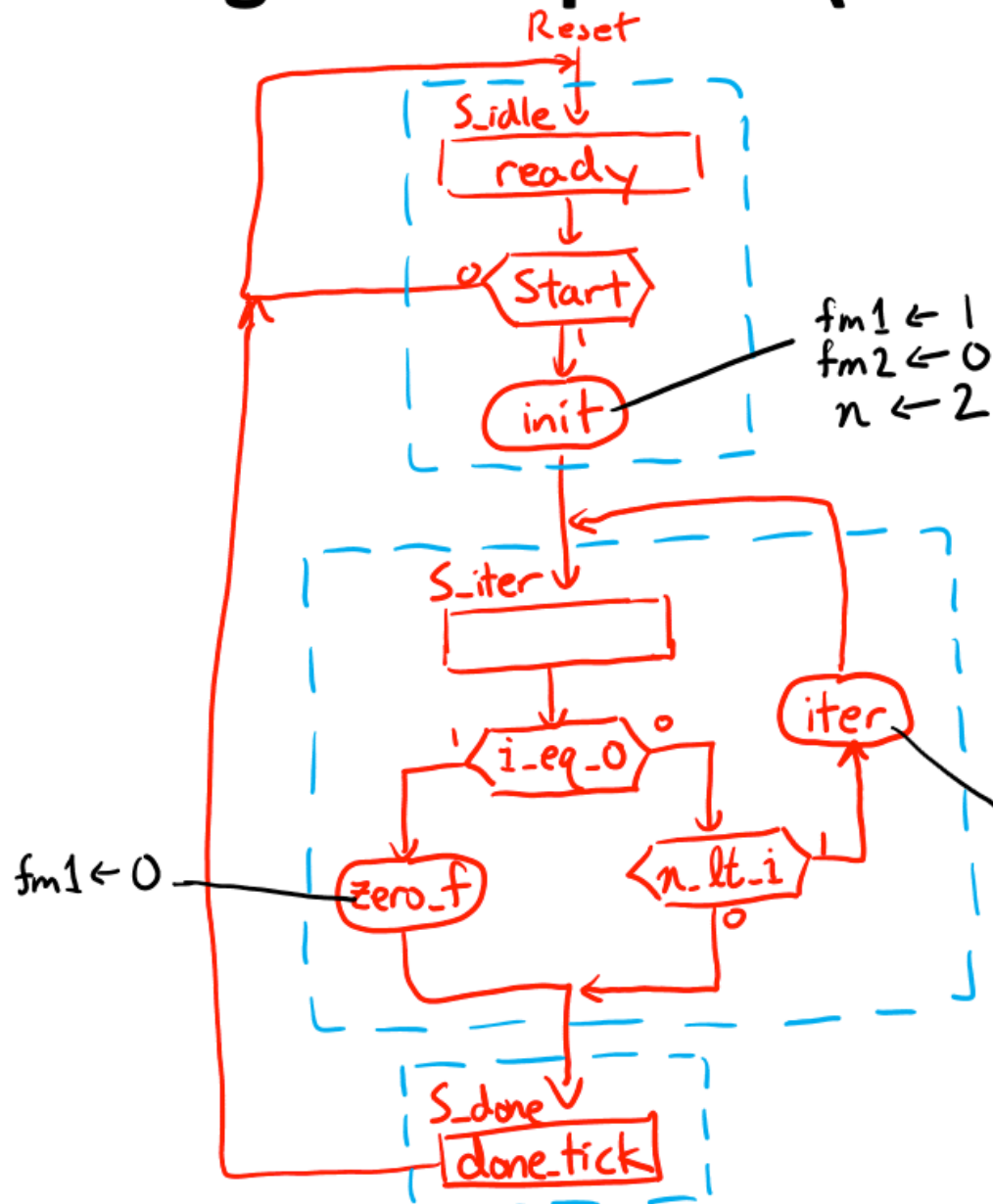

Some Variants:

- $i == 0$ check could be in **S_idle**
- n could count down
- **done_tick** could be a Mealy output from **S_comp** (shows up 1 cycle earlier)
- f could be a separate register from $fm1$ & $fm2$ and be updated just once

$fm2 \leftarrow fm1$
 $fm1 \leftarrow fm1 + fm2$
 $n \leftarrow n + 1$

Design Example #2 (SV)

```
fib_control:
    // port definitions
    // define state names and variables
    // controller logic w/synchronous reset
    // next state logic
    // output assignments

fib_datapath:
    // port definitions
    // datapath logic

fib:
    // port definitions
    // define status and control signals
    // instantiate control and datapath
```


Other Hardware Algorithms

- ❖ Sequential binary multiplier or divider
- ❖ Arithmetic mean
- ❖ Lab 4: Bit counting
- ❖ Lab 4: Binary search
- ❖ Lab 5: Bresenham's line

Hardware Acceleration

- ❖ ASMD as a design process can be used to implement software algorithms
- ❖ Custom hardware can accelerate operation:
 - Hardware can better exploit parallelism
 - Hardware can implement more specialized operations
 - Hardware can reduce “processor overhead”
(*e.g.*, instruction fetch, decoding)
- ❖ “Hardware accelerators” are frequently used to complement processors to speed up common, computationally-intensive tasks
 - *e.g.*, encryption, machine vision, cryptocurrency mining

❖ Multiplication of unsigned numbers

(b) Using multiple adders

c) Hardware implementation

Parallel Binary Multiplier

❖ *Parallel* multipliers require a lot of hardware

