 


# FSM Example: String Manipulator

- ❖ Takes in a stream of inputs and removes the *second* 1 from every consecutive string of 1's.



input:    0 1 1 0 0 1 1 1 0 0 1

out:      0 1 0 0 0 1 0 1 1 0 0 1

# String Manipulator FSM

```
module fsm (input logic clk, reset, in,
            output logic out);
```

```
    // present and next state
```

```
    enum {S0, S1, S3} ps, ns;
```

```
    // next state logic
```

```
    always_comb
```

```
        case (ps)
```

```
            S0: if (in) ns = S1;
```

```
                else ns = S0;
```

```
            S1: if (in) ns = S3;
```

```
                else ns = S0;
```

```
            S3: if (in) ns = S3;
```

```
                else ns = S0;
```

```
        endcase
```

```
    // output logic
```

```
    assign out = in & (ps[1] | ~ps[0]);
```

```
    ...
```

```
    ...
```

```
    // sequential logic (DFFs)
```

```
    // synchronous reset
```

```
    always_ff @(posedge clk)
```


```
        if (reset)
```

```
            ps <= S0; // reset state
```

```
        else
```

```
            ps <= ns;
```

```
endmodule // fsm
```

 

# Moore vs. Mealy



- ❖ **Moore** machines define their outputs based on states ( $\textcircled{00/1}$ ) and **Mealy** machines define outputs based on transitions ( $\xrightarrow{0/1}$ )
  - Mealy machines are more *flexible*
    - Moore outputs are function of state; Mealy outputs are function of state *and inputs*
  - All FSMs can be expressed in either form, but some systems are more naturally expressed one way versus the other
    - Feel free to use either in this class if not specified
    - However, there *are* implementation differences!

# Mealy $\leftrightarrow$ Moore Conversions

Not testable  
material

- ❖ **Moore  $\rightarrow$  Mealy:** copy the state output to every transition *entering* the state

  - ❖ Example: FSM for a *turnstile*, which is locked until someone swipes their Husky ID (input H) and then locks once you push through (input P) the unlocked gate. Outputs a light that glows red (0) or green (1).




# Mealy $\leftrightarrow$ Moore Conversions

Not testable  
material

- ❖ **Mealy  $\rightarrow$  Moore:** more complicated process; if incoming transitions differ in output, may need to “split” the state

 
- ❖ Example: the threeOnes FSM from Lecture 1



# Moore vs. Mealy Outputs

- ❖ Compare a Moore and Mealy FSM for the turnstile. Complete the statements and waveform below, assuming no delays:


Moore:

 


```

assign out_moore = (ps == U);
assign out_mealy = H & ~P & (ps == L) |
                  (ps == U) & ~P;
  
```

Mealy:

 

 
$$H \cdot \bar{P} \cdot \bar{ps} + ps \cdot \bar{P} \checkmark$$




# Moore vs. Mealy Outputs

## ❖ Moore:

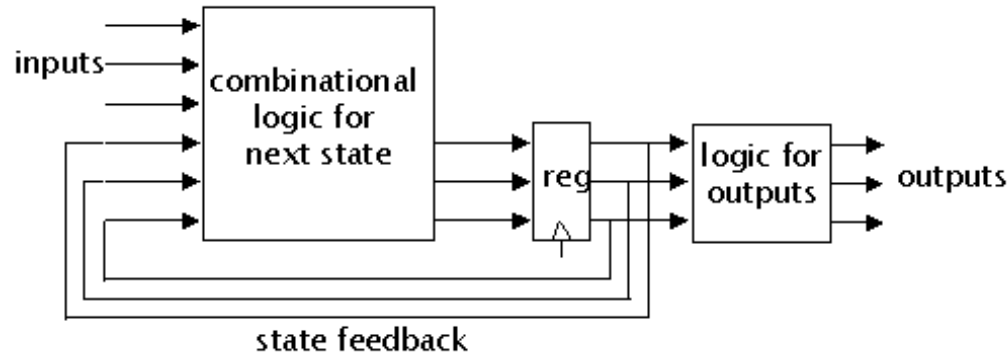

- Outputs change synchronously with state changes

## ❖ Mealy:

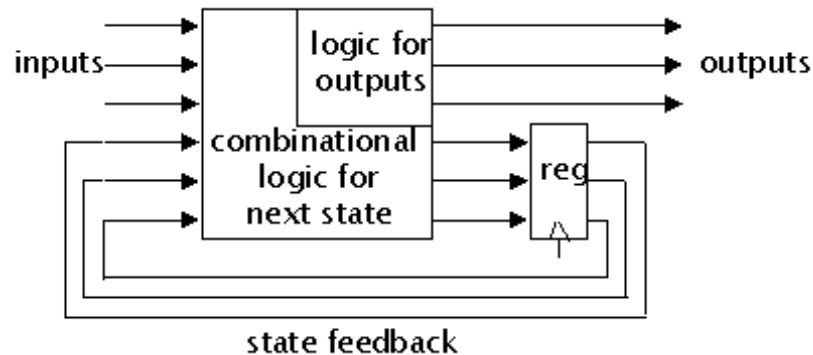

- Input changes can cause *immediate* output changes



# Lecture Outline

- ❖ SystemVerilog Review & Tips (Cont.)
- ❖ Finite State Machine Design
- ❖ **Testbenches**

# Testbenches

- ❖ Special modules *needed for simulation only!*
  - Software constraint to mimic hardware
- ❖ ModelSim runs entirely on your computer
  - Tries to simulate your FPGA environment without actually using hardware – no physical signals available
  - Must create fake inputs for FPGA's physical connections
    - *e.g.*, LEDR, HEX, KEY, SW, CLOCK\_50
  - Unnecessary when code is loaded onto FPGA
- ❖ Need to define both input signal combinations as well as their *timing*

# Testbench Timing Controls

*#10*

*# (period/2);*

- ❖ Delay: #<time>
  - Delays by a specific amount of simulation time
- ❖ Edge-sensitive: @( <pos/neg>edge <signal> )
  - Delays next statement until specified transition on signal
- ❖ Level-sensitive Event: wait(<expression>)
  - Waits until <expression> evaluates to TRUE
- ❖ Stop simulation: \$stop;
  - \$ finish .*
- ❖ Timescale: `timescale <time unit> / <precision>
  - e.g., `timescale 1 ns / 1 ps

# Extender Testbench

Zero  
Sign


MSB 0/1

```
`timescale 1 ns / 1 ns
module extender_tb();

    parameter M = 4, N = 8;
    logic [M-1:0] in;
    logic [N-1:0] out;
    logic sign;

    extender #(M, N) dut (.*) ;

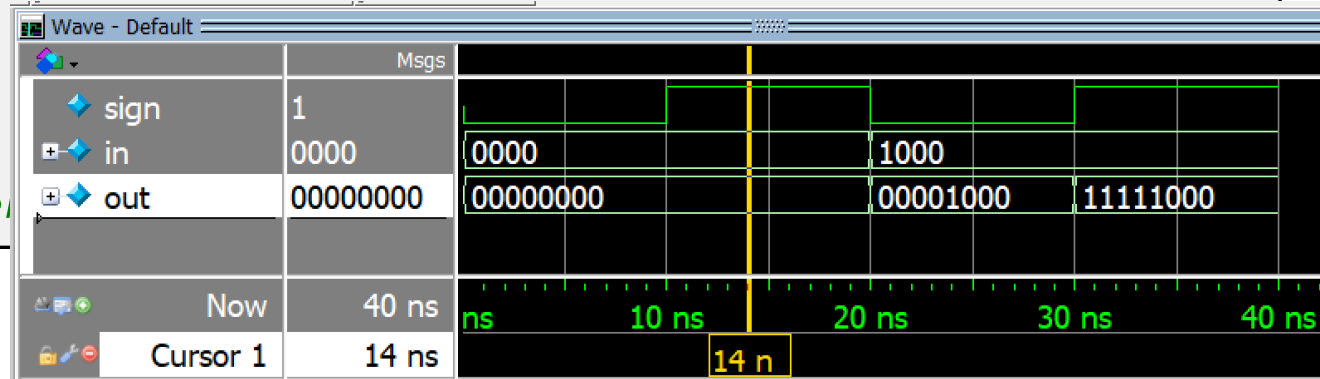    int i;
    initial begin
        for (i = 0; i < 2**2; i++) begin
            sign = i[0]; in = {i[1], {(M-1){1'b0}}}; #10;
        end // for
        $stop;
    end // initial
endmodule // extender_tb
```



# FSM Testbench Notes

- ❖ Your main goal is to test *every transition* that we care about – may take extra clock cycles
- ❖ For simulation, you need to generate a clock signal
  - Assume we have `parameter clock_period;`

**Explicit  
Edges:**

```
initial
    clk = 0;

always_comb begin
    #(clock_period/2) clk <= 1;
    #(clock_period/2) clk <= 0;
end
```

**Toggle:**

```
initial begin
    clk <= 0;
    forever #(clock_period/2) clk <= ~clk;
end
```

# String Manipulator Testbench

```

module fsm_tb();
    logic clk, reset, in, out;

    fsm dut (.*);

    // simulated clock
    parameter period = 100;
    initial begin
        clk <= 0;
        forever
            #(period/2)
            clk <= ~clk;
    end // initial clock

    ...

```

```

...



initial begin
    reset <= 1; @posedge clk;
    reset <= 0; in <= 0; @posedge clk;
    in <= 0; @posedge clk;
    in <= 1; @posedge clk;
    in <= 0; @posedge clk;
    in <= 1; @posedge clk;
    in <= 1; @posedge clk;
    in <= 0; @posedge clk;
    in <= 1; @posedge clk;
    in <= 1; @posedge clk;
    in <= 1; @posedge clk;
    @posedge clk;

    $stop; // end simulation
end // initial signals

endmodule // fsm_tb

```

# String Manipulator Waveforms

  

# Checking Responses

- ❖ Visually checking simulated waveforms quickly becomes impractical for large designs simulated over thousands of clock cycles
  - Displaying and explaining your waveforms for labs can be tedious
- ❖ There are simulator-independent system tasks to write messages to the user/tester!
  - Look similar to `printf()` in C
    - `$<system_task>(<format_string>, <sig_1>, <sig_2>, ...)`
  - Will look at `$display` today and others later on



# Checking Responses: \$display

- ❖ Triggers once when encountered, prints the given format string and adds a new line:

```
// define test inputs
int i;
initial begin
    for (i = 0; i < 2**2; i++) begin
        sign = i[0]; in = {i[1], {(M-1){1'b0}}}; #10;
        $display("t = %0t, %b %s %b",
            $time, in, sign ? "-+->" : "-0->", out);
    end // for
    $stop;
end // initial
```

Transcript

```
VSIM O>
# t = 10, 0000 -0-> 00000000
# t = 20, 0000 -+-> 00000000
# t = 30, 1000 -0-> 00001000
# t = 40, 1000 -+-> 11111000
```

# Format Specifiers

Table 5.7: Format Specifiers.

Specifier	Meaning
%h	Hexadecimal format
%d	Decimal format
%o	Octal format
%b	Binary format
%c	ASCII character format
%v	Net signalstrength
%m	Hierarchical name of current scope
%s	String
%t	Time
%e	Real in exponential format
%f	Real in decimal format
%g	Real in exponential or decimal format

Table 5.8: Special characters.

Symbol	Meaning
\n	New line
\t	Tab
\\	\character
\"	" character
\xyz	Where xyz is are octal digits - the character given by that octal code
%%	% character

- **Warning:** these differ from the specifiers for `printf`
- The *minimum* field width is specified by numbers between the '%' and specifier letter
  - e.g., %3d will pad out to 3 digits if necessary,  
%0d will show just the minimum number of digits needed

EE/CSE 371  
Design of Digital Circuits and Systems

Lecture 3: Memory I

## Relevant Course Information

1. HW 1 and Lab 1 due this week

2. Demos are in progress

~~3~~ 2. HW 2 and Lab 2 will be posted on Wednesday October 4th


4. Online lectures next week.

# Review Question

- ❖ Design a FSM that will output two consecutive 1's any time it sees the string "010" and outputs 0 otherwise
  - 1 input bit and 1 output bit
  - How many state bits do we need?
  - Which state should be your initial/reset state?
  
- ❖ If you have time, design both a **Moore** machine and **Mealy** machine "from scratch" (*i.e.*, don't convert between the two)
  - Which seems easier to implement? Can you name specific ways that the SystemVerilog implementation will be "easier"?
 
# Review Solution

- ❖ Design a FSM that will output two consecutive 1's any time it sees the string "010" and outputs 0 otherwise



Moore

Do after class

# Aside: Powers of 2 and Prefixes

- ❖ Here focusing on large numbers (*i.e.*, exponents  $> 0$ )
- ❖ SI prefixes are *ambiguous* if base 10 or 2
  - Note that  $10^3 \approx 2^{10}$   
                   1000           1024
- ❖ IEC prefixes are *unambiguously* base 2

**SIZE PREFIXES ( $10^x$  for Disk, Communication;  $2^x$  for Memory)**

SI Size	Prefix	Symbol	IEC Size	Prefix	Symbol
$10^3$	Kilo-	K	$2^{10}$	Kibi-	Ki
$10^6$	Mega-	M	$2^{20}$	Mebi-	Mi
$10^9$	Giga-	G	$2^{30}$	Gibi-	Gi
$10^{12}$	Tera-	T	$2^{40}$	Tebi-	Ti
$10^{15}$	Peta-	P	$2^{50}$	Pebi-	Pi
$10^{18}$	Exa-	E	$2^{60}$	Exbi-	Ei
$10^{21}$	Zetta-	Z	$2^{70}$	Zebi-	Zi
$10^{24}$	Yotta-	Y	$2^{80}$	Yobi-	Yi

$2^0 = 1$
$2^1 = 2$
$2^2 = 4$
$2^3 = 8$
$2^4 = 16$
$2^5 = 32$
$2^6 = 64$
$2^7 = 128$
$2^8 = 256$
$2^9 = 512$
$2^{10} = 1024$

# Memory

- ❖ Several forms of memory are available, which include:
  - ~~Secondary memory (e.g., hard disk, flash drive)~~
  - Read-only memory (ROM)
  - Random-access memory (RAM)
  - Register files
    - Small, fast, fixed-sized memory that hold CPU data state
  - First in, first out (FIFO) buffers



# Embedded FPGA Memory

- ❖ An FPGA contains prefabricated memory modules
  - Intended for small or intermediate-sized storage
  - Contents of memory blocks can be configured via memory initialization files (*.mif*)
- ❖ The DE1-SoC's Cyclone V FPGA (Cyclone V SE A5) has:
  - 31k Adaptive Logic Modules (ALMs)
  - 4.45 Mbits of memory organized as 397 memory blocks, each with 10 kbits of storage (M10K)
    - Flexible, configurable memory storage available to the designer
    - Each M10K can act as single-port memory, dual-port RAM, shift register, ROM, or a FIFO buffer
  - More info in “*Cyclone V Device Handbook Vol 1.pdf*”

# DE1-SoC Memory


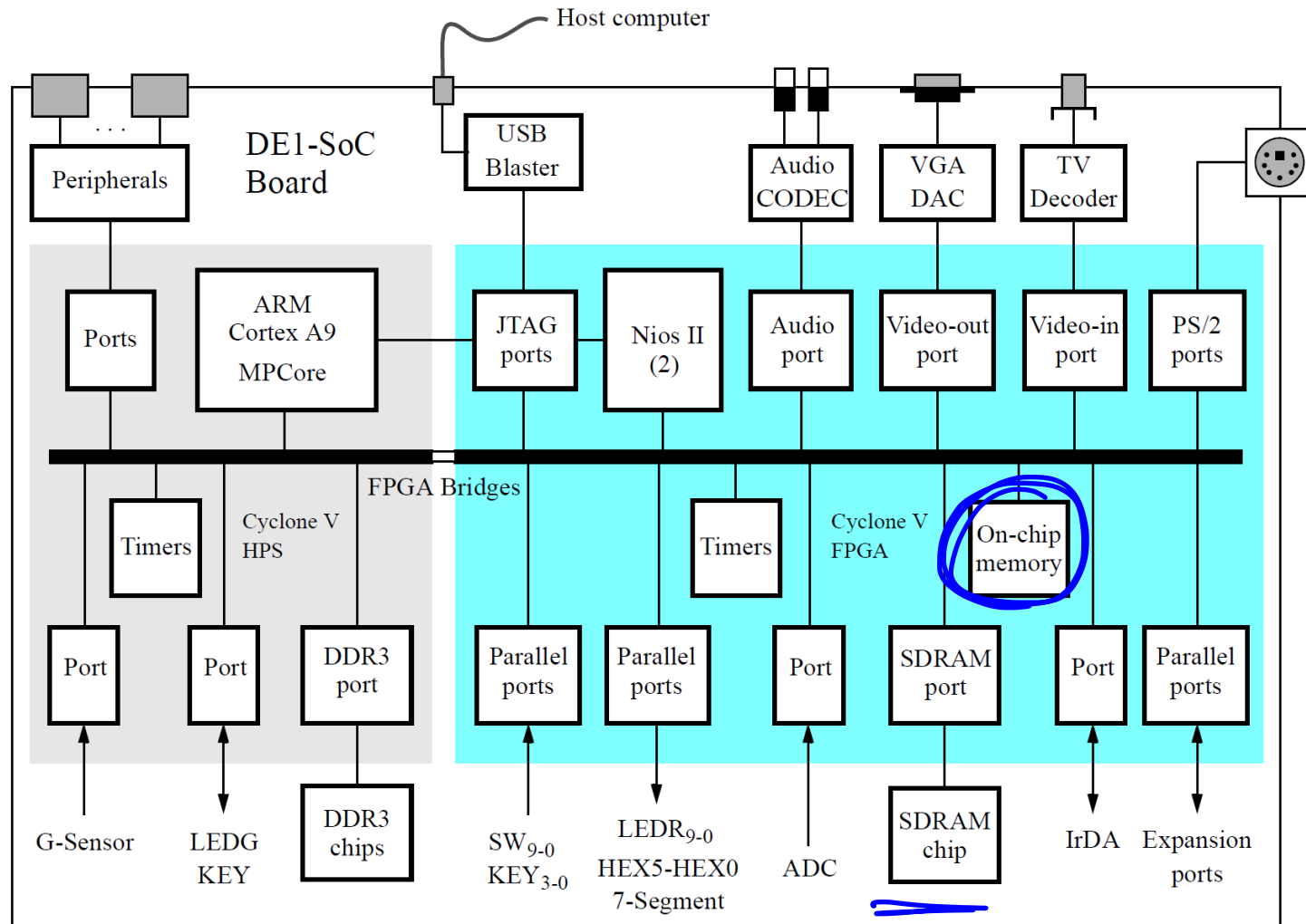


Figure 1. Block diagram of the DE1-SoC Computer.


# Cyclone V Adaptive Logic Modules

[https://www.altera.com/content/dam/altera-www/global/en\\_US/pdfs/literature/hb/cyclone-v/cv\\_5v2.pdf](https://www.altera.com/content/dam/altera-www/global/en_US/pdfs/literature/hb/cyclone-v/cv_5v2.pdf)

Figure 1-5: ALM High-Level Block Diagram for Cyclone V Devices

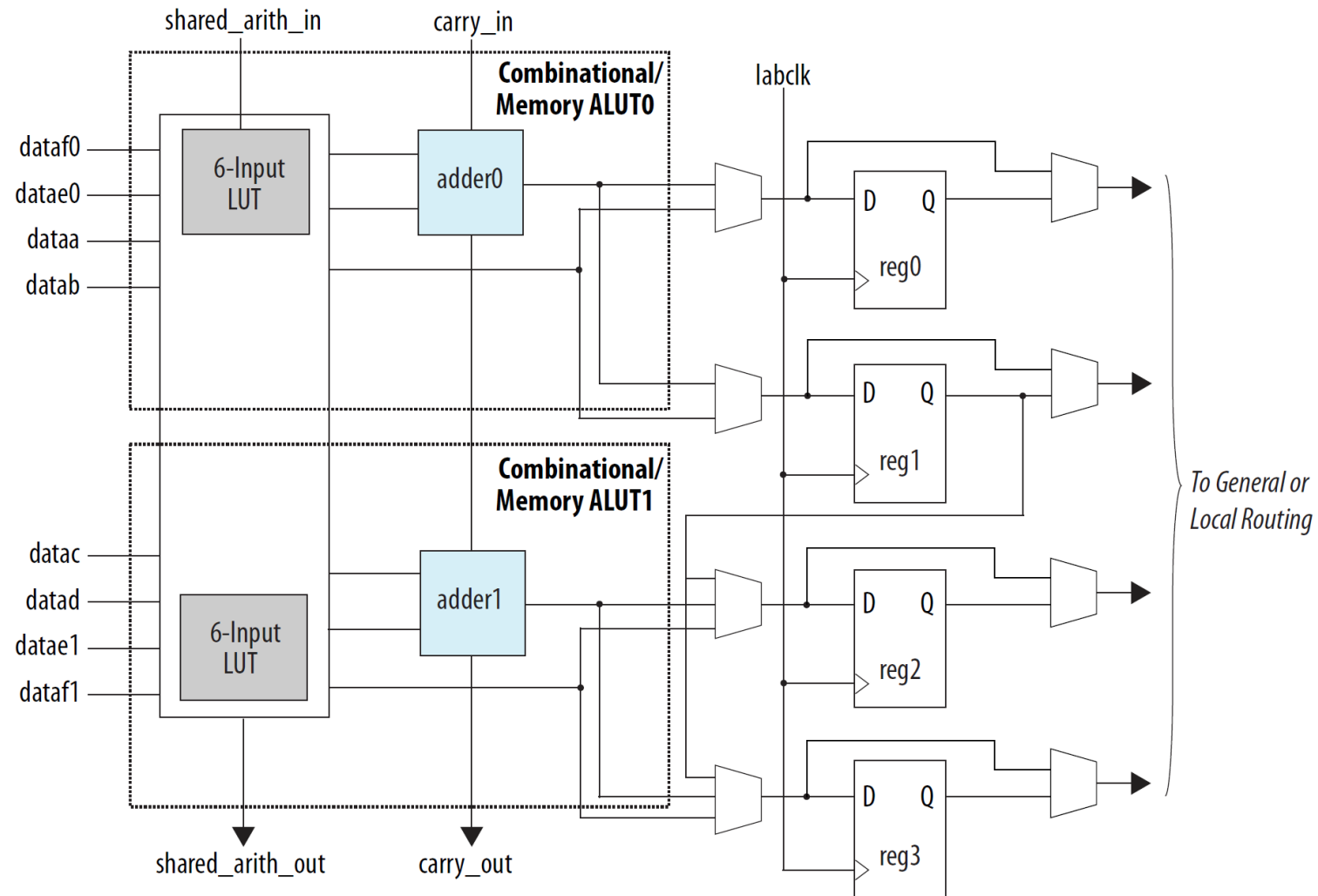


# Memory Modules

 
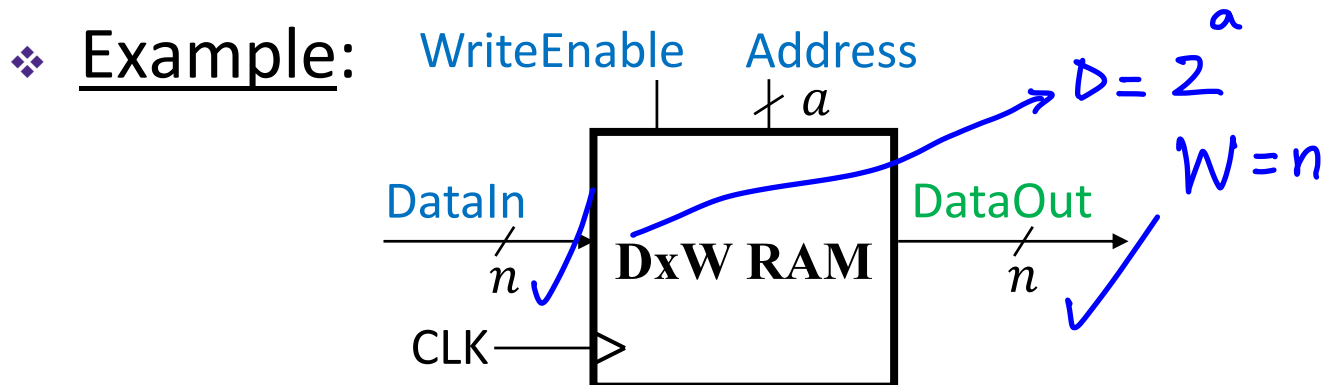
## ❖ Key characteristics of a simple memory module:

- Width – the number of bits in a word
- Depth – the number words in the module
- Number of ports
- Synchronicity of port access – whether or not accesses are controlled by a clock signal
- Simultaneous address access – can the same address be used for both read and write operations



# Memory Characteristics

- ❖ Memory units are specified as **depth**  $\times$  **width**.
- ❖ For the following memory units, answer:
  - 1) Memory capacity (in bits and bytes using IEC prefixes)
  - 2) Width of address bus
  - 3) Width of data output bus

$$1 \text{ byte} = 8 \text{ bits} \\ = 2^3 \text{ bits}$$

❖ Memory 1:  $\underline{8\text{Ki}} \times \underline{32}$

$\xrightarrow{2^3} \quad \xrightarrow{2^{10}} \quad \xrightarrow{2^5}$   
 $\underset{d}{\quad} \quad \quad \underset{w}{\quad}$

$$1. \quad 2^{18} \text{ bits} = 2^{15} \text{ bytes} \\ = 32 \text{ KiB}$$

$$2. \quad 13 \text{ bits.}$$

$$3. \quad 32 \text{ bits.}$$

❖ Memory 2:  $\underline{2\text{Gi}} \times \underline{8}$

$\downarrow \quad \downarrow \quad \downarrow$   
 $2^1 \quad 2^{30} \quad 2^3$

$$1. \quad 2^{34} \text{ bits} = 2^{31} \text{ bytes} \\ = 2 \text{ GiB}$$

$$2. \quad 31 \text{ bits}$$

$$3. \quad 8 \text{ bits.}$$

# Technology Break

# Memory Type #1: ROM

## ❖ Read-Only Memory

- A purely *combinational* circuit (no internal state)
- Output is determined solely by address input


## ❖ In an FPGA:

- No actual embedded ROM, but can be emulated by a combinational circuit or a RAM with the write operation disabled
- Only practical for small tables

## ❖ In SystemVerilog:



- Define the ROM content as a 2-dimensional constant
- Oftentimes a selected assignment or case statement

# Example ROM

 

❖ Hex-to-7seg LED decoder:

- Segments:
  - Active low

  

❖ ROM size?

16 x 7

B3	B2	B1	B0	L0	L1	L2	L3	L4	L5	L6
0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	1	0	0	1	1	1	1
0	0	1	0	0	0	1	0	0	1	0
		⋮					⋮			
1	1	0	1	1	0	0	0	0	1	0
1	1	1	0	0	1	1	0	0	0	0
1	1	1	1	0	1	1	1	0	0	0



# Example ROM (SystemVerilog)

```
module ROM_case(addr, data);
```

```
endmodule
```

# Example ROM (SystemVerilog)


```

module ROM_case(addr, data);
    input  logic [3:0] addr;
    output logic [6:0] data;

    always_comb
        case (addr)
            // 0000
            4'h0: data = 7'b1000000;
            4'h1: data = 7'b1111001;
            4'h2: data = 7'b0100100;
            // ...
            4'hD: data = 7'b0100001;
            4'hE: data = 7'b0000110;
            4'hF: data = 7'b0001110;
        endcase
    endmodule

```

lx

 

# Reading Data from a File

- ❖ Hard-coded values in your SV files can be tedious to format, debug, and swap out!
- ❖ Verilog provides *system tasks* to read data from a text file into an array: `$readmemb()` and `$readmemh()`
  - Basic usage: `$readmemb("file.txt", my_array);`
  - Reads in numerals (in **b**inary or **h**ex) from file separated by *whitespace* (*i.e.*, spaces, tabs, newlines)
  - Can avoid some recompilation
  - File can have any extension
  - Be very careful with dimensions of array and ordering of data in file!



# Example ROM (SystemVerilog)

```

module ROM_file(addr, data);
    input  logic [3:0] addr;
    output logic [6:0] data;

    logic [6:0] ROM [0:15]; // (!) unpacked dimension
    initial
        // reads binary values from file into array
        $readmemb("seg7decode.txt", ROM);

    assign data = ROM[addr];
endmodule

```

seg7decode.txt:

10000000	1111001	0100100	0110000
0011001	0010010	0000010	1111000
0000000	0010000	0001000	0000011
1000110	0100001	0000110	0001110

# Dynamic Array Indexing Operation

- ❖ A signal can be used as an index to access an element in the array:

```
assign data = ROM[addr];
```

equivalent to

```
always_comb
  case (addr)
    4'h0: data = ROM[0];
    4'h1: data = ROM[1];
    // ...
    4'hE: data = ROM[14];
    4'hF: data = ROM[15];
  endcase
```

# Synchronicity Revisited



- ❖ To synchronize either the address input or ROM output, we can add a register as appropriate
  - Sometimes called “registering” the input or output to make your module “synchronous”
  - In SystemVerilog, can be done inside or outside of the module:

```
initial
    $readmemb("seg7decode.txt", ROM);

// internally-registered ROM module
always_ff @(posedge clk)
    data <= ROM[addr];
```