


❖ Multiplication of unsigned numbers

(b) Using multiple adders

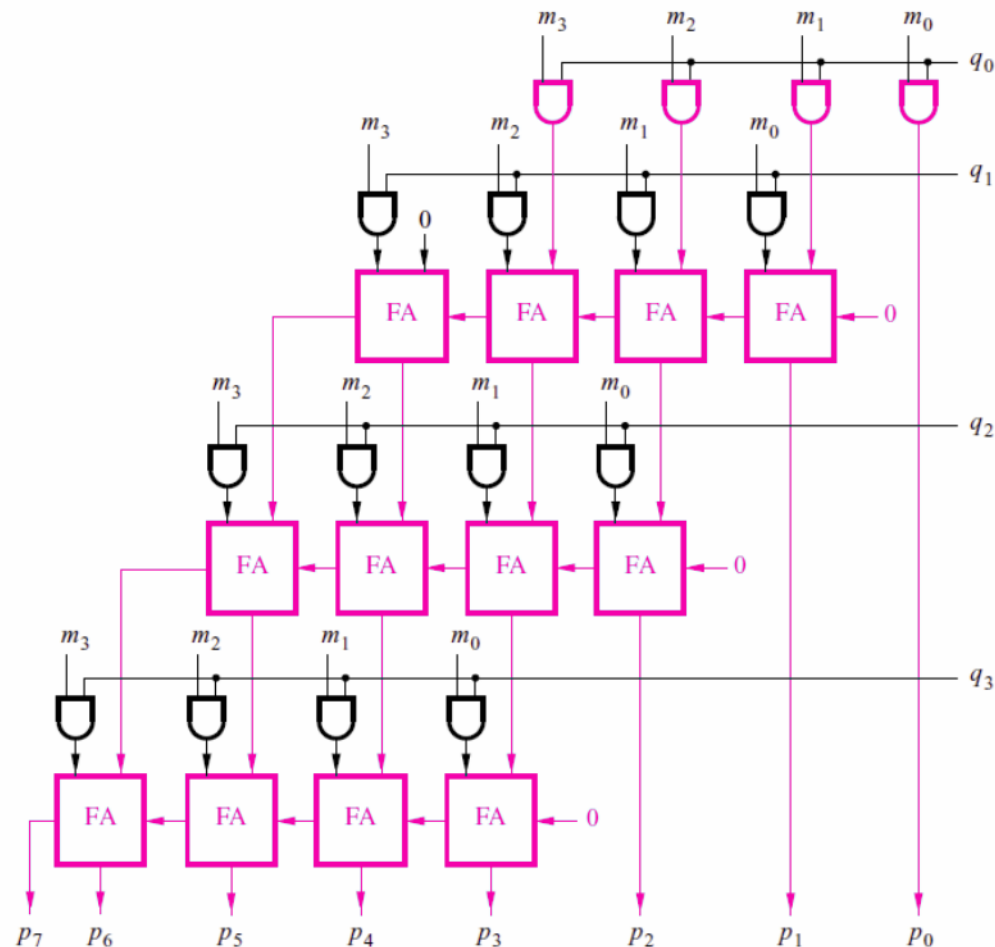c) Hardware implementation

Parallel Binary Multiplier

❖ *Parallel* multipliers require a lot of hardware




Sequential Binary Multiplier

- ❖ Design a *sequential* multiplier that uses **only one adder** and a **shift register**
 - Assume one clock cycle to shift and one clock cycle to add
 - More efficient in hardware, less efficient in time

- ❖ Considerations:

 - n -bit **multiplicand** and **multiplier** yield a product at most how wide? *$2n$ - bits for product.*
- What are the ports for an n -bit adder?
- How many shift-and-adds do we do and how do we know when to stop? *n - times.*



Counter
initialize to n
count down.

Sequential Binary Multiplier

- ❖ Design a *sequential* multiplier that uses only one adder and a shift register
 - Assume one clock cycle to shift and one clock cycle to add
 - More efficient in hardware, less efficient in time
- ❖ Implementation Notes:
 - If current bit of **multiplier** is 0, then skip the adding step
 - Instead of shifting **multiplicand** to the left, we will shift the **partial sum** (and the **multiplier**) *to the right*
 - We will re-use the **multiplier** register for the lower half of the product
 - Treat **carry**, **partial sum**, and **multiplier** as one shift register {C, A, Q}


Partial Sum
Multiplier
↓ ↓
C A Q
2n+1

Sequential Binary Multiplier Operation

❖ A few steps of:

B → 11010111

Q → X 00010111

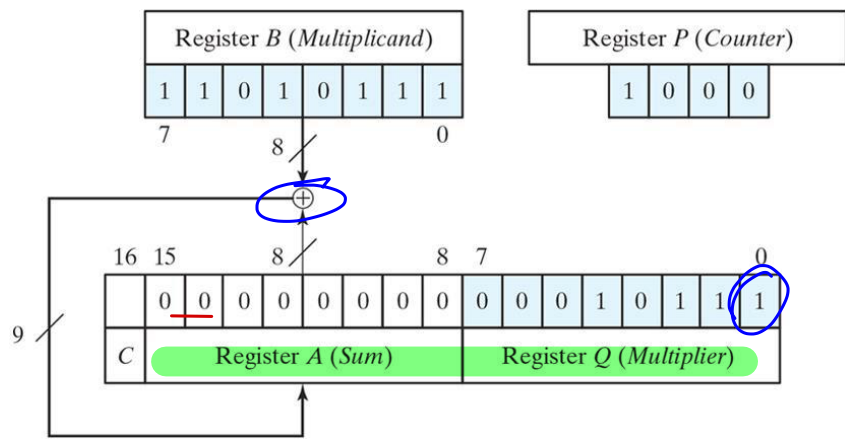

Operation (completed)	C	A	Q	P
Initialize computation	0	00000000	00010111	1000
Add (Q[0] = 1)	0	11010111	00010111	0111
Shift	0	01101011	10001011	0111
Add (Q[0] = 1)	1	01000010	10001011	0110
Shift	0	10100001	01000101	0110

IEEE - 754

$10^{\pm 308}$

64 bits.

1

sign

11

exponent

52

fraction.

Binary Multiplier Specification

❖ Datapath

- $(2n+1)$ -bit *shift register* with bits split into 1-bit C , n -bit A , and n -bit Q
- Multiplicand stored in register B , multiplier stored in Q
- An n -bit *parallel adder* adds the contents of B to A and outputs to $\{C, A\}$
- A $\lceil \log_2(n + 1) \rceil$ -bit *counter* P

❖ Control

external inputs


status indicators

- Inputs $Start$ and $Reset$, outputs $Ready$ and $Done$

Decision ■ Status signals: $Q[0]$, P_zero



Action ■ Control signals: Add_regs , $Shift_regs$, $\underbrace{Load_regs}_{init}$, $Decr_P$

Binary Multiplier Block Diagram

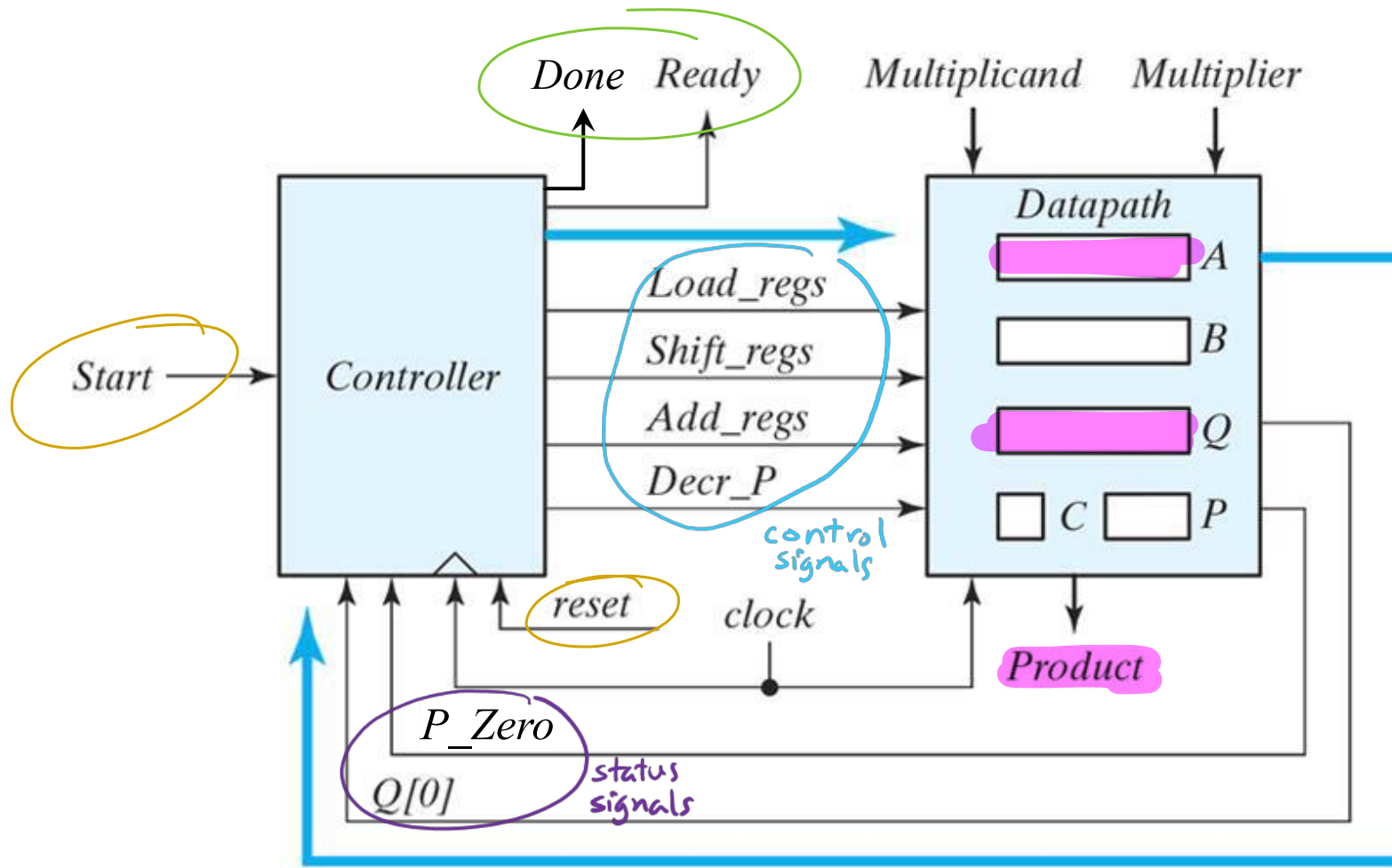

Binary Multiplier (ASMD Chart)

State Outline

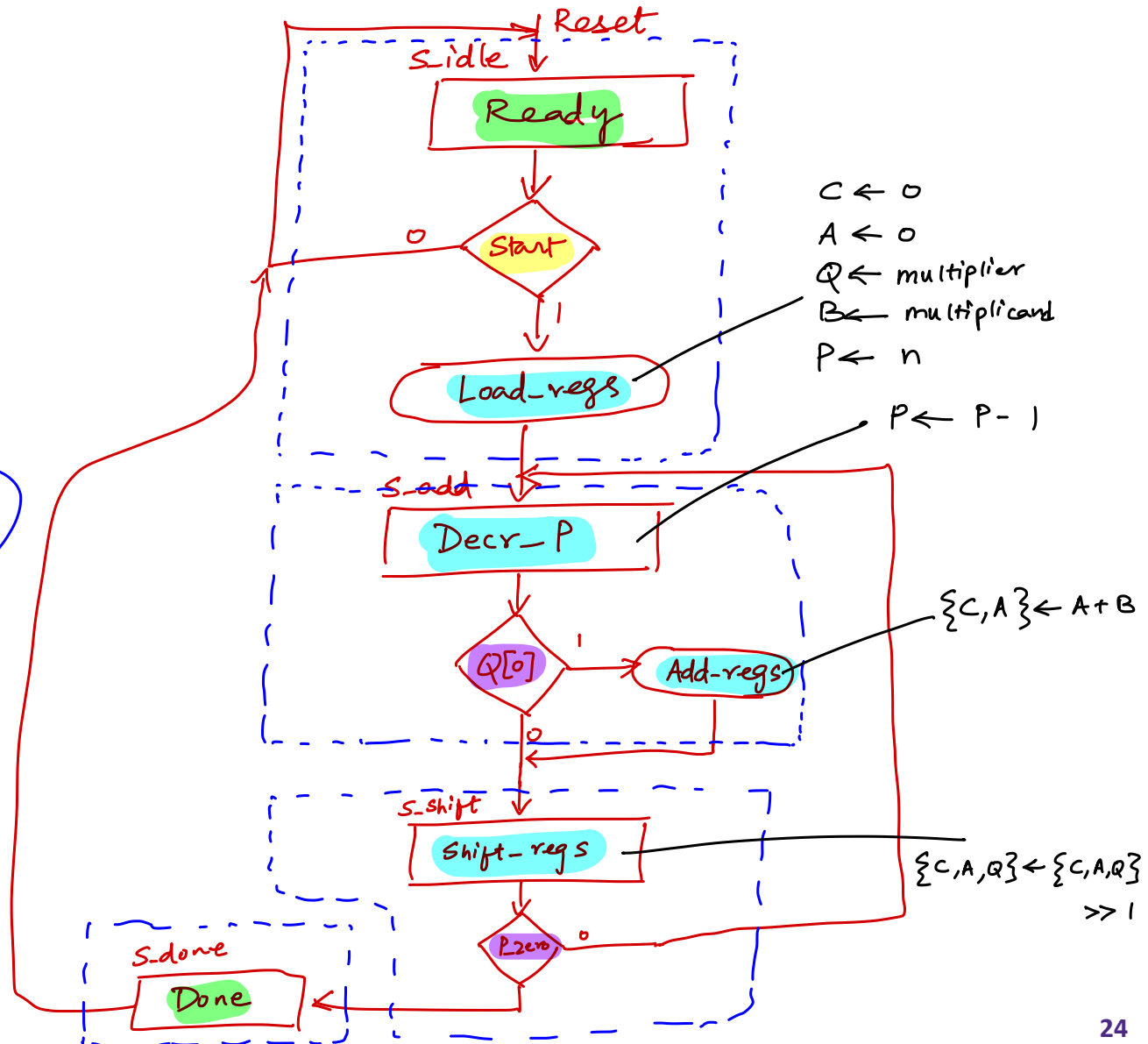 

Binary Multiplier Implementation

❖ Controller Logic

$Load_regs = S_idle \& Start$

$Shift_regs = S_shift$

$Add_regs = S_add \& Q[0]$

$Decr_P = S_add$

$Ready = S_idle$

$Done = S_done.$

Binary Multiplier (SV, Datapath)

```
module datapath #(parameter WIDTH=8)
    (product, Q, P, multiplicand, multiplier, clk,
     Load_regs, Shift_regs, Add_regs, Decr_P);

    // port definitions
    output logic [2*WIDTH-1:0] product;
    output logic [WIDTH-1:0] Q, P; // note: unnecessary bits for P
    input  logic [WIDTH-1:0] multiplicand, multiplier;
    input  logic clk, Load_regs, Shift_regs, Add_regs, Decr_P;

    // internal logic
    logic C;
    logic [WIDTH-1:0] A, B;

    // datapath logic

endmodule
```

Binary Multiplier (SV, Datapath)

```
module datapath #(parameter WIDTH=8)
    (product, Q, P, multiplicand, multiplier, clk,
     Load_regs, Shift_regs, Add_regs, Decr_P);

    // port definitions
    ...

    // internal logic
    ...

    // datapath logic
    always_ff @(posedge clk) begin
        if (Load_regs) begin
            A <= 0; C <= 0; P <= WIDTH;
            B <= multiplicand;
            Q <= multiplier;
        end
        if (Decr_P)      P <= P - 1;
        if (Add_regs)    {C, A} <= A + B;
        if (Shift_regs) {C, A, Q} <= {C, A, Q} >> 1;
    end // always_ff


    assign product = {A, Q};

endmodule
```

EE/CSE 371
Design of Digital Circuits and Systems

Lecture 8: Algorithms to Hardware I

ASMD Chart Review Questions

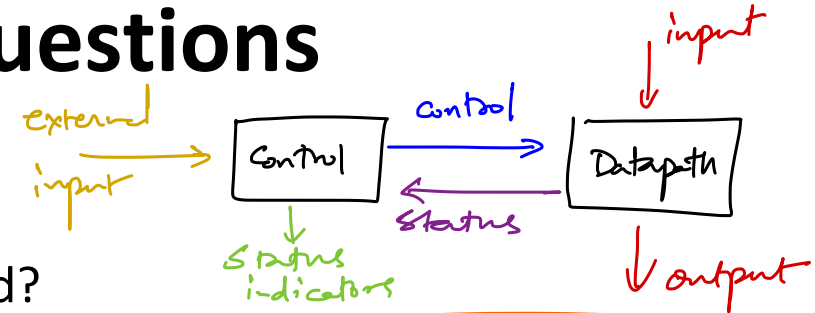

❖ Circle all that apply: *outputs*

- ① Where can **control signals** be found?
 - a* State boxes
 - b* Decision boxes
 - c* Conditional output boxes
- ② Where can **status signals** be found? *inputs*
 - a* State boxes
 - b* Decision boxes
 - c* Conditional output boxes
- ③ Where can **external input signals** be found?
 - a* State boxes
 - b* Decision boxes
 - c* Conditional output boxes
- ④ What is the *first* thing a path should encounter in an **ASM block**?
 - a* State boxes
 - b* Decision boxes
 - c* Conditional output boxes
- ⑤ What can be found outside of **ASM blocks**? *None!*
 - a* State boxes
 - b* Decision boxes
 - c* Conditional output boxes
- ⑥ What can **RTL operations** be attached to?
 - a* Control signals
 - b* Status signals
 - c* External output signals

ASMD Process Review

- 1) Identify datapath components, control signals, and status signals from description or pseudocode.
- 2) [*optional*] Create control-datapath circuit diagram.
- 3) [*optional*] Create state outline to plan out states and transitions between them.
- 4) Draw out ASM state boxes, decision boxes, and paths between them.
- 5) Augment state boxes with Moore-type outputs and add conditional output boxes with Mealy-type outputs.
- 6) Add ASM blocks to organize states.
- 7) Add RTL operations to control signals.
- 8) Double-check decision box edge cases and timing of operations (*i.e.*, debug).

Division Circuit

- ❖ Design a circuit that implements the long-division algorithm:

$$\begin{array}{r} 15 \\ 9 \overline{) 140} \\ \underline{9} \\ 50 \\ \underline{45} \\ 5 \end{array}$$

(a) An example using decimal numbers

$$\begin{array}{r} \text{divisor} \rightarrow 1001 \quad \begin{array}{r} 00001111 \\ 1001 \overline{) 10001100} \\ \underline{1001} \\ 10001 \\ \underline{1001} \\ 10000 \\ \underline{1001} \\ 1110 \\ \underline{1001} \\ 101 \end{array} \begin{array}{l} \leftarrow \text{quotient} \\ \leftarrow \text{dividend} \\ \leftarrow \text{remainder} \end{array} \end{array}$$

(b) Using binary numbers


- ❖ Considerations:

- Main operations? *Subtract, shift, compare*
- Stop condition? *n iterations if both divisor & dividend are n-bits.*

Division Circuit

- ❖ Design a circuit that implements the long-division algorithm:
 - 1) Double the **dividend** width by appending 0's in front and align the **divisor** to the leftmost bit of the *extended dividend*.
 - 2) If the corresponding **dividend** bits are \geq the **divisor**, subtract the **divisor** from the **dividend** bits and make the corresponding **quotient** bit 1. Otherwise, keep the original **dividend** bits and make the **quotient** bit 0.
 - 3) Append one additional **dividend** bit to the previous result and shift the divisor to the right one position.
 - 4) Repeat steps 2 and 3 until all dividend bits are used.

Division Circuit

 

❖ Implementation Notes:

- If current **dividend window** is smaller than the **divisor**, skip subtraction
- Instead of shifting **divisor** to the right, we will shift the **dividend** (and the **quotient**) *to the left*
- We will re-use the lower half of the **dividend** register to store the **quotient**