


EE/CSE 371
Design of Digital Circuits and Systems

Lecture 6: ASM with Datapath I


Relevant Course Information

1. Homework 3 due Wednesday (10/18)
2. Lab 3 due Friday (10/27)


Review: ASM Chart

 


(a) State box

 

(b) Decision box

 

(c) Conditional output box


 


(d) ASM block

Review Question: 3-way Switch

❖ Create an ASM chart for a 3-way switch system using *Mealy*-type output

  
- LTog and RTog pulse 1 when switch is flipped/toggled, output called `light`



ASMD Charts

- ❖ An **A**lgorithmic **S**tate **M**achine with a **D**atapath chart is created by adding RTL operations to an ASM chart
 - Timing of operations can be confusing – *NOT* a flowchart
- ❖ School of Thought #1:
 - RTL operations are triggered by control signals, so they can appear anywhere an output signal can:

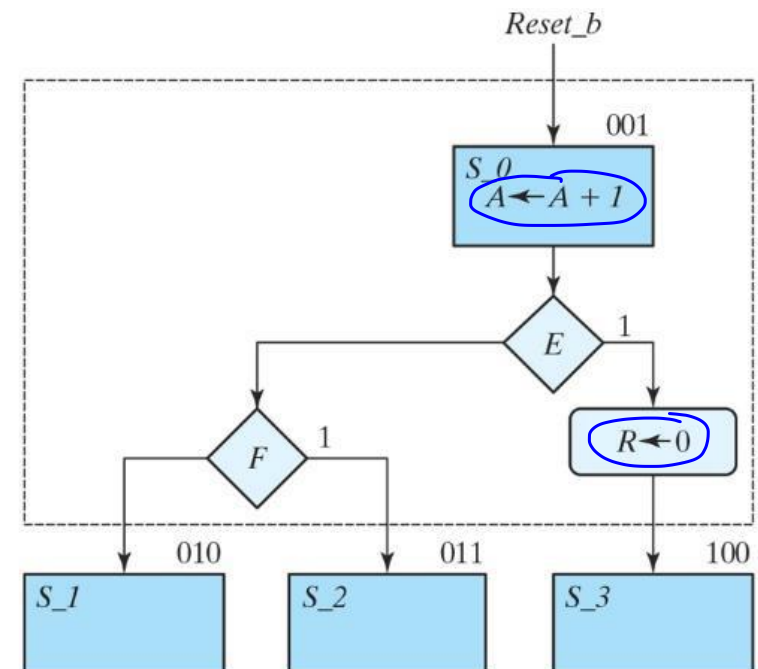missing
control
signals
that
are
asserted.




ASMD Charts

- ❖ An **A**lgorithmic **S**tate **M**achine with a **D**atapath chart is created by adding RTL operations to an ASM chart
 - Timing of operations can be confusing – *NOT* a flowchart


- ❖ School of Thought #2:
 - It's clearer to separate control signals (Control) from RTL operations (Datapath)

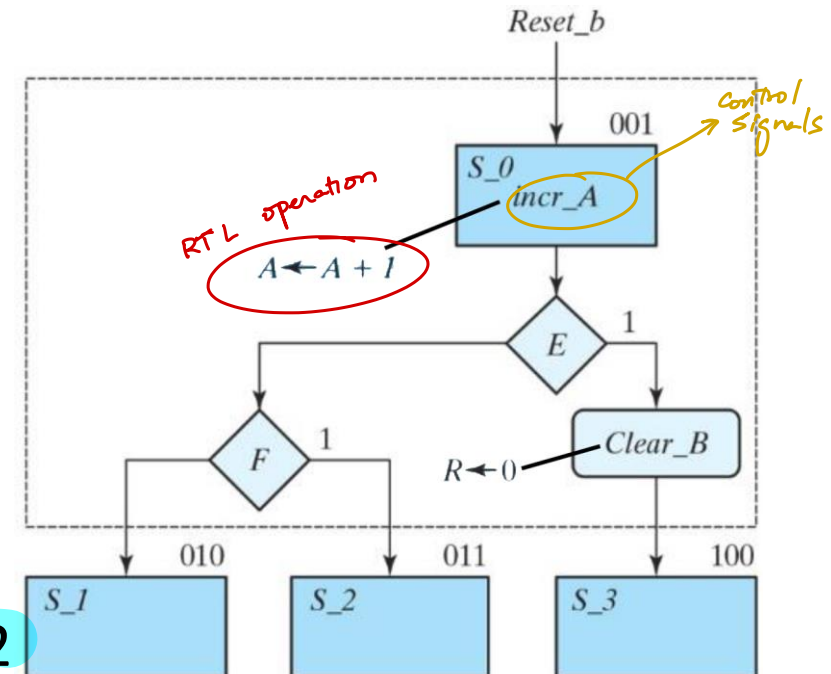- ❖ There isn't a set standard
 - You may see both or variants
 - I will use School of Thought #2



ASMD Hardware

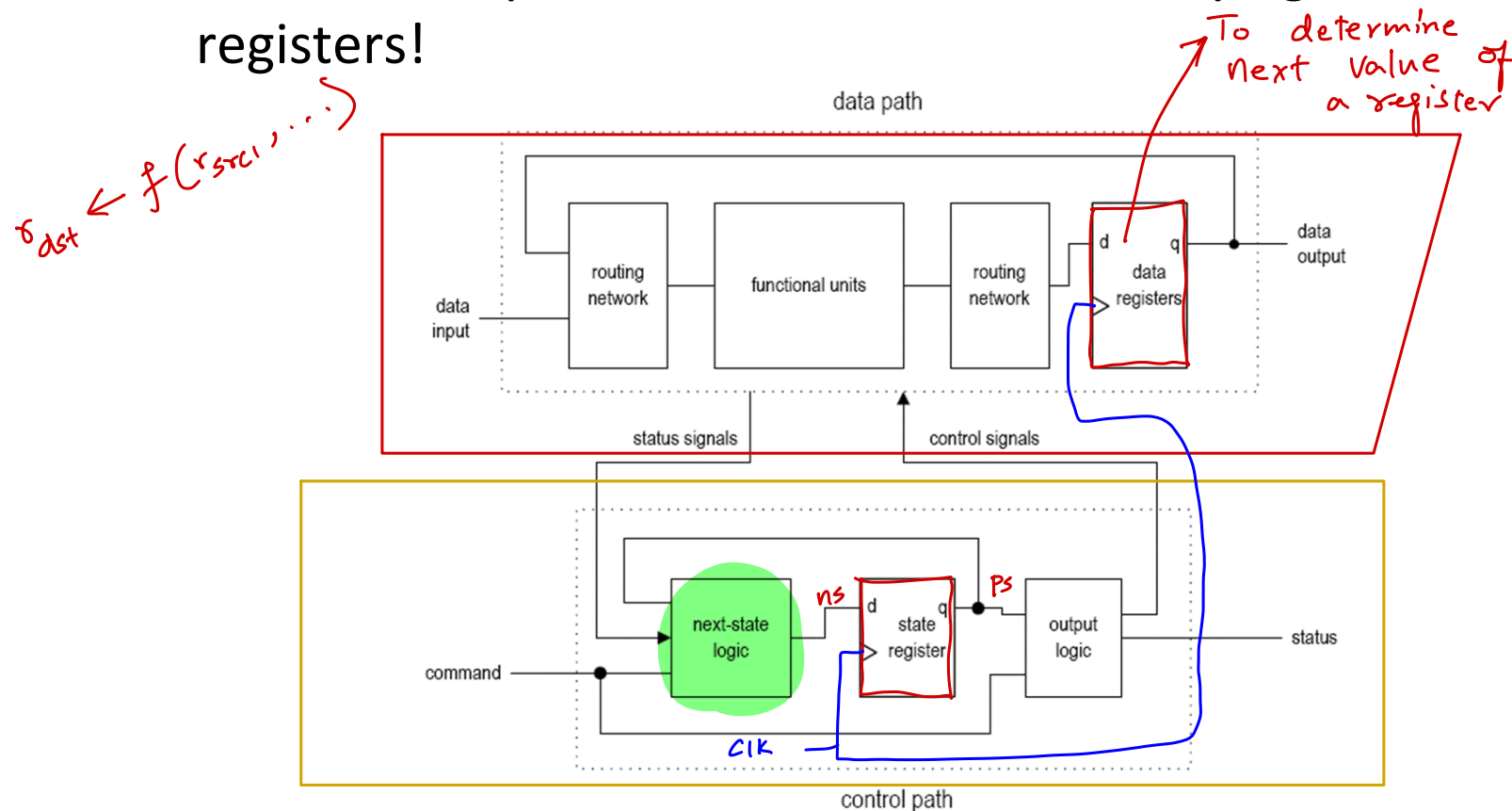- ❖ State transitions and RTL operations are both controlled by the clock
- It's often helpful to remember the underlying hardware – registers!




ASMD Hardware

Control

Datapath.

- ❖ State transitions and RTL operations are both controlled by the clock
 - It's often helpful to remember the underlying hardware – registers!
- ❖ The behavior of both state and data registers depend on the current control state
 - Can conceptually think of as a MUX to the registers' inputs that uses the current state as its selector bits

next slide


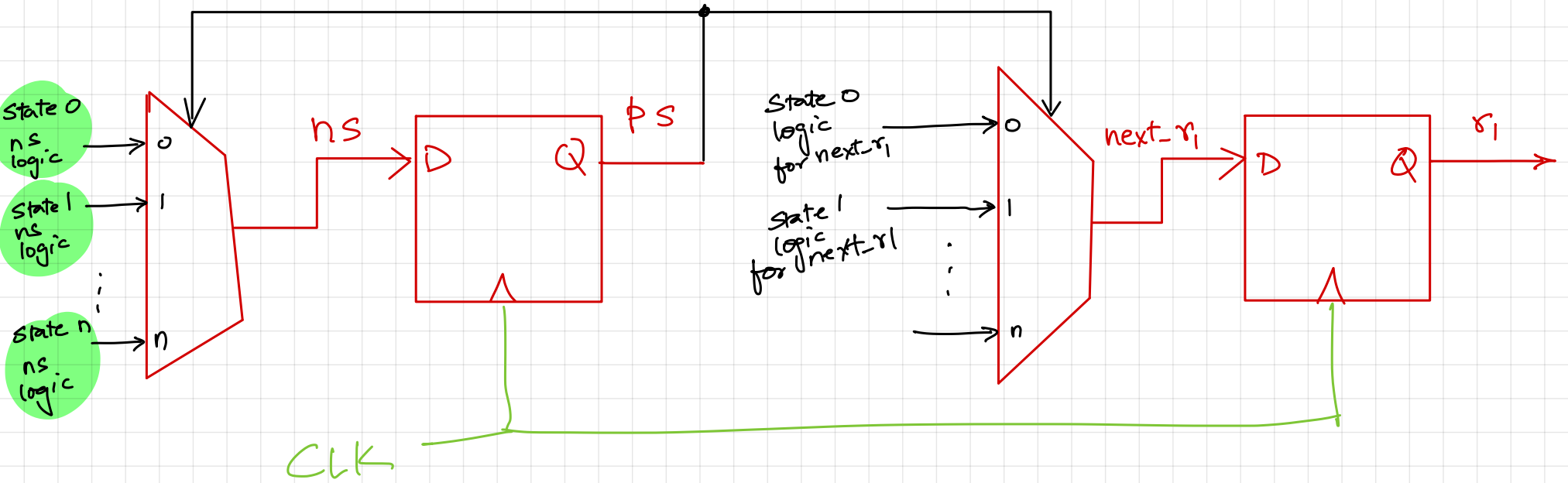


Control

Datapath.



Hardware Example #1

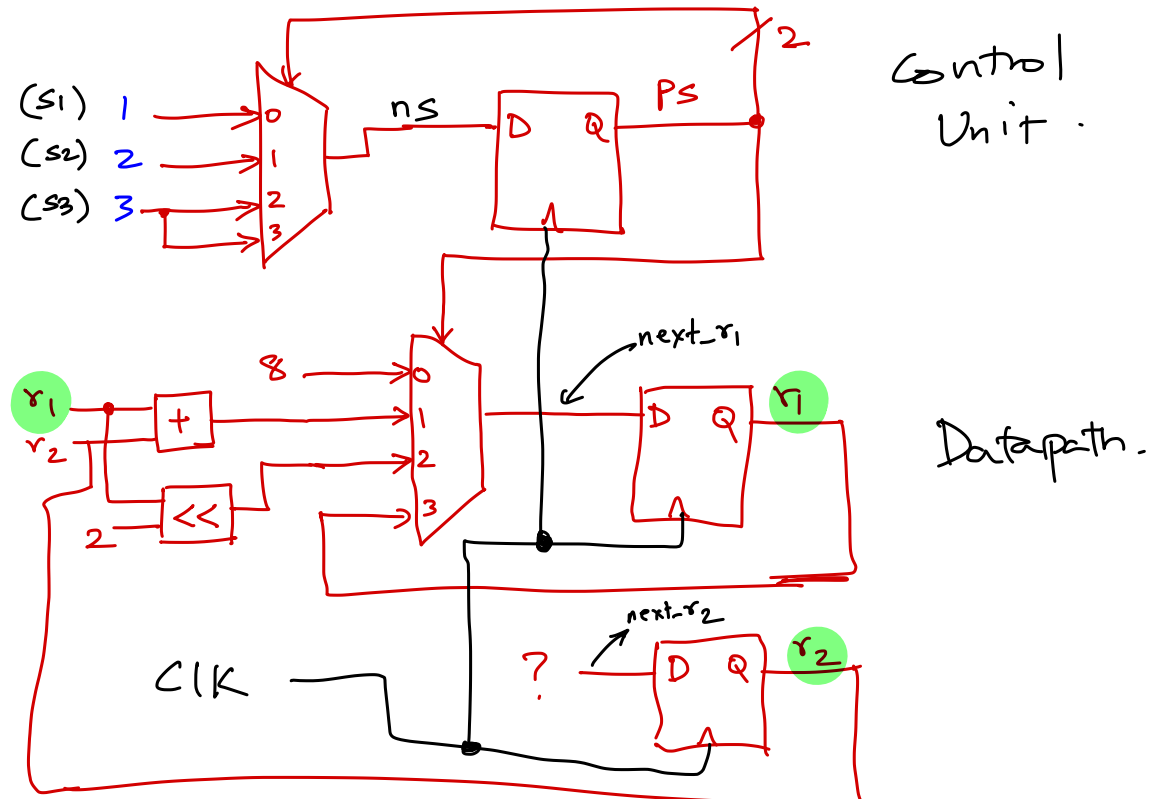 - ❖ State transitions and RTL operations are both controlled by the clock
 - It's often helpful to remember the underlying hardware – registers!





Hardware Example #2

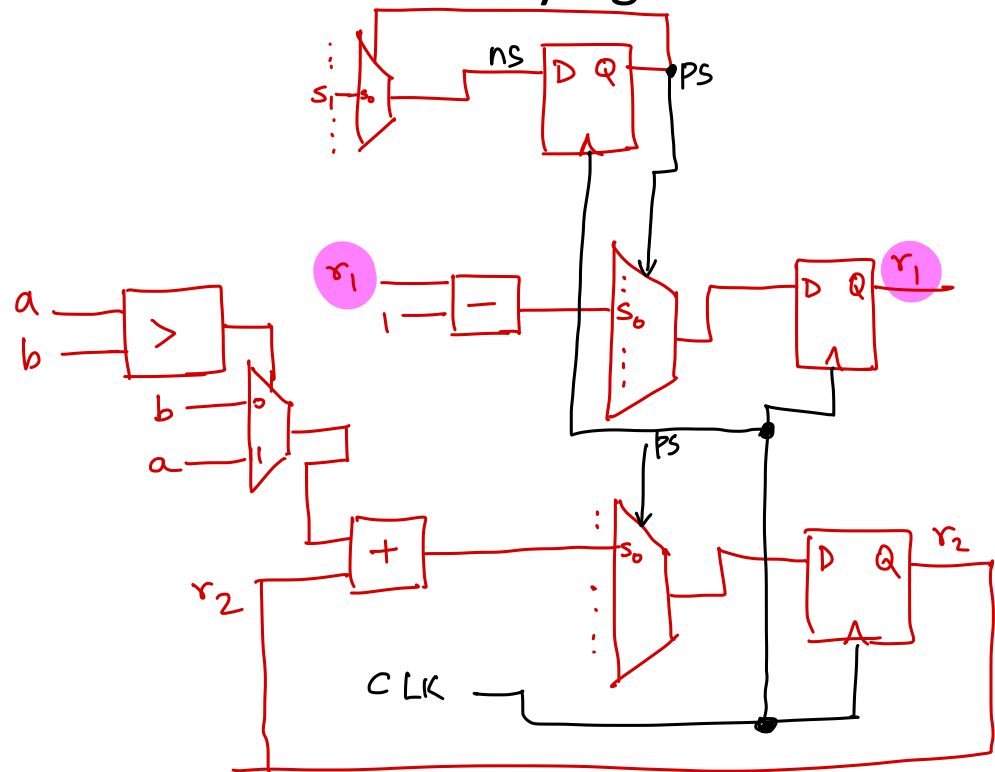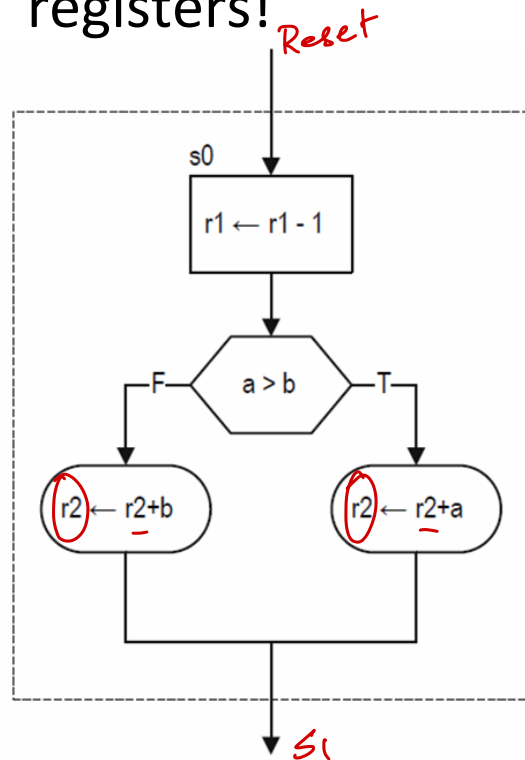- ❖ State transitions and RTL operations are both controlled by the clock
- It's often helpful to remember the underlying hardware – registers!





ASMD Timing

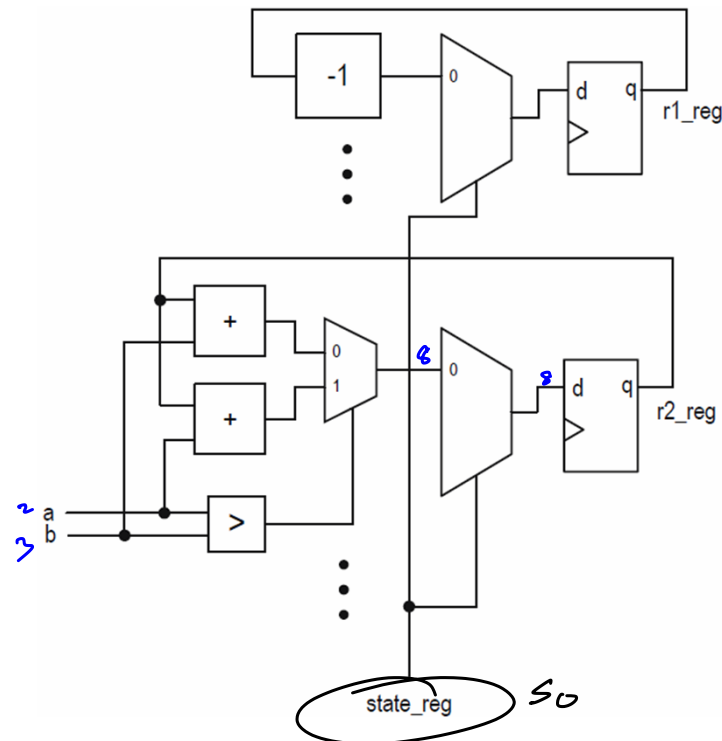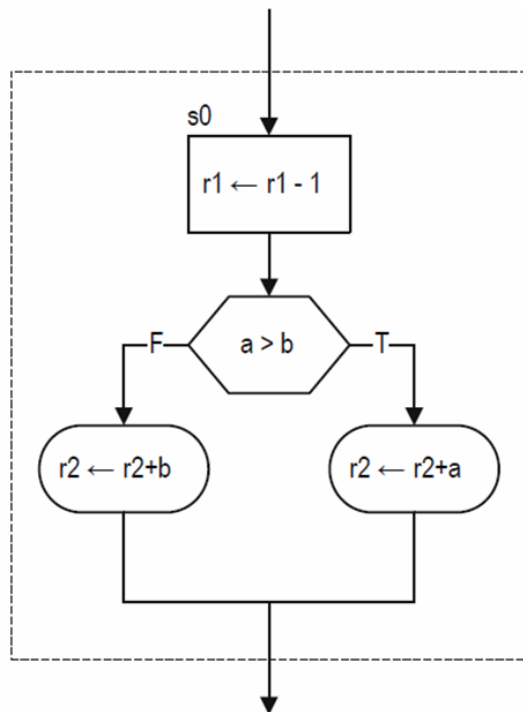- ❖ Everything (registers!) within an ASM block occurs simultaneously at the next clock trigger
 - Differs from a flowchart – changes occur at state exit rather than *entrance*




ASMD Timing

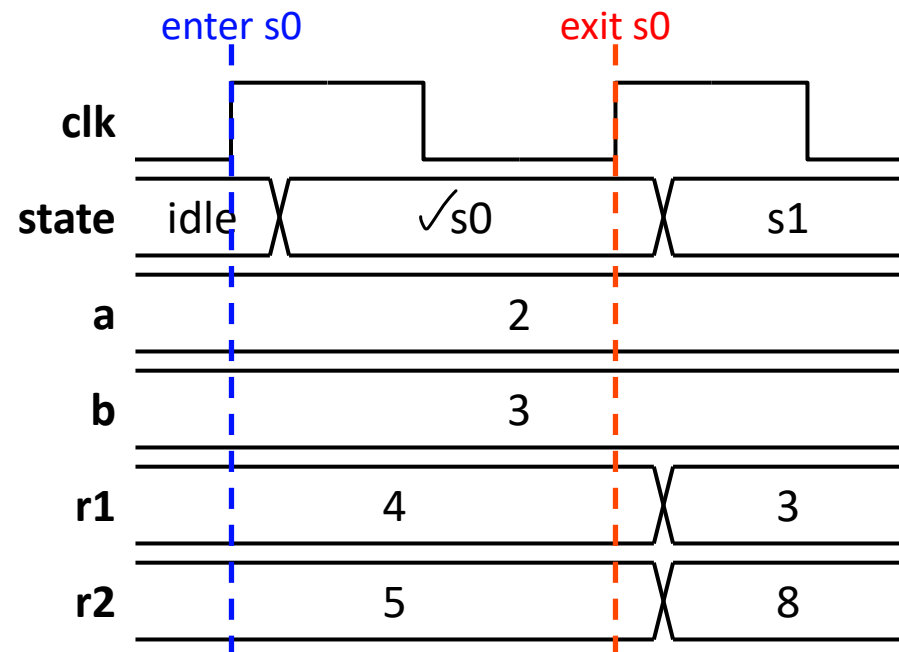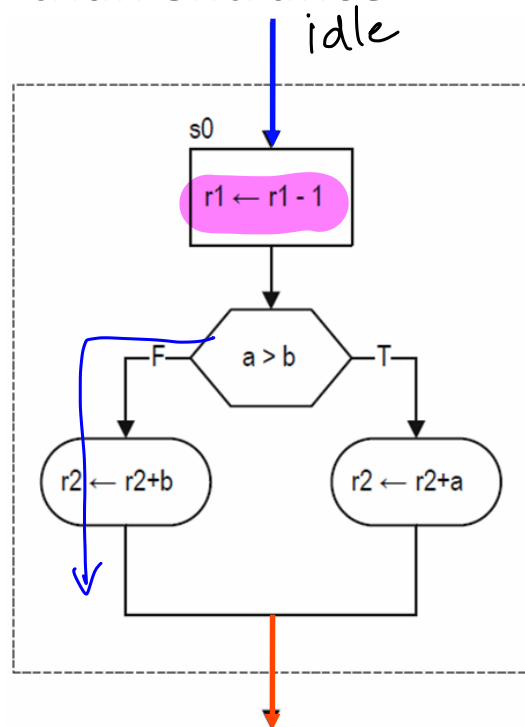- ❖ Everything (registers!) within an ASM block occurs simultaneously at the next clock trigger
 - Differs from a flowchart – changes occur at state exit rather than *entrance*




ASMD Timing Question

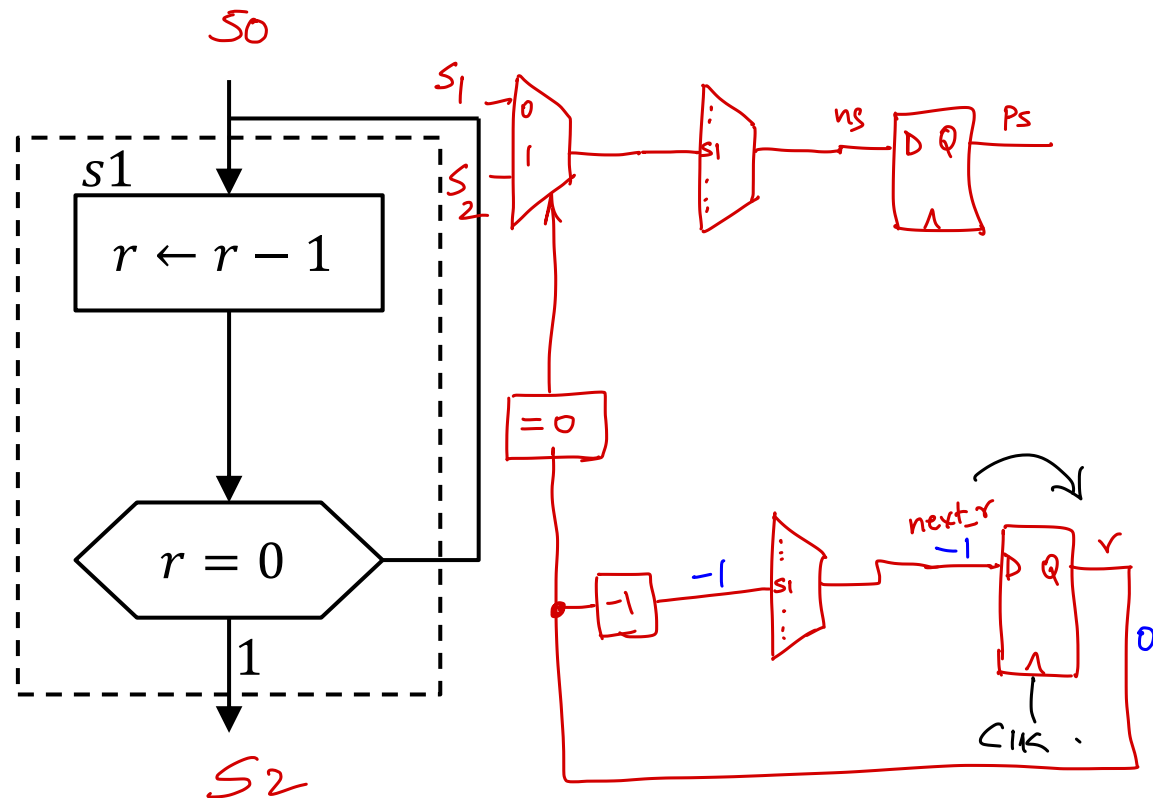- ❖ What value will be stored in r when we transition from state $s1$ to the next state? -1 , 0 , 1



ASMD Timing

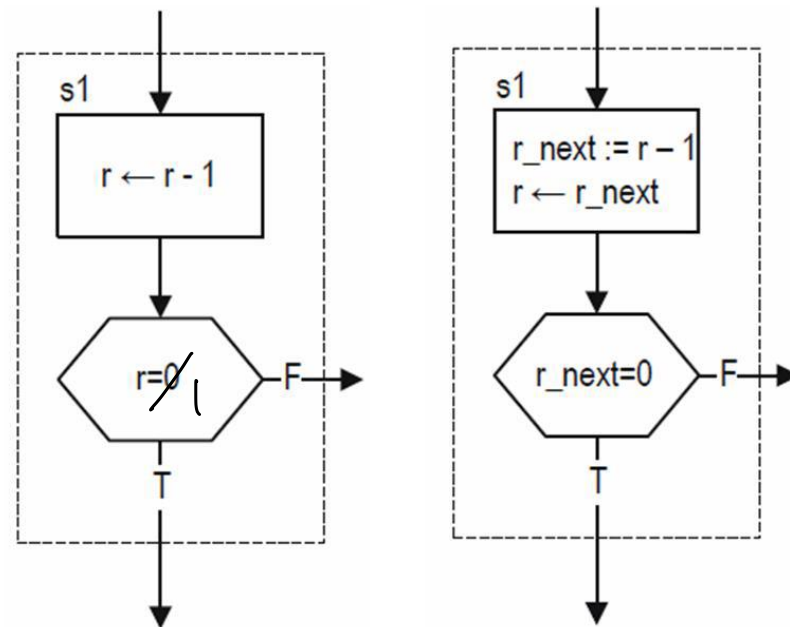- ❖ When a registered output (*e.g.*, r) is used in a decision box, its effect may appear to be delayed by one clock
- Can define a next-state value (*e.g.*, r_next) to use instead



(a) Use old value of r (b) Use new value of r

Short Tech Break


ASMD Design Procedure

- ❖ From problem description or algorithm pseudocode:
 - 1) **Identify necessary datapath components and operations**
 - 2) **Identify states and signals that cause state transitions**
(external inputs and status signals), based on the necessary sequencing of operations
 - 3) **Name the control signals** that are generated by the controller that cause the indicated operations in the datapath unit
 - 4) **Form an ASM chart for your controller**, using states, decision boxes, and signals determined above
 - 5) **Add the datapath RTL operations** associated with each control signal

Control

Design Example #1


❖ System specification:

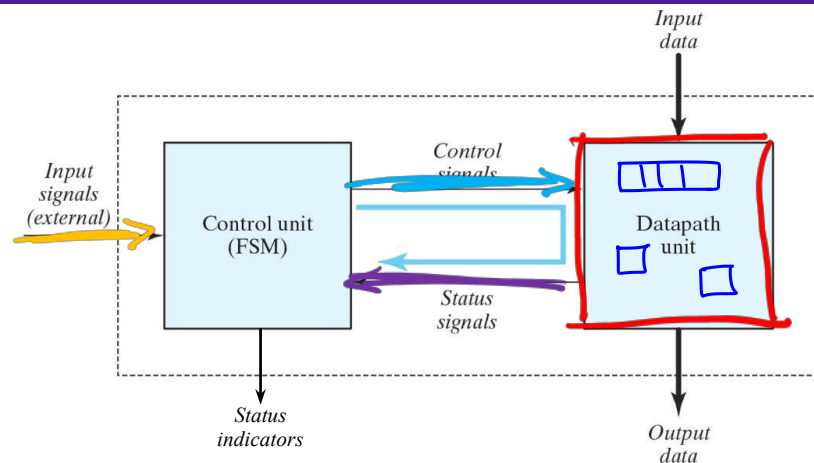

- datapath
 - Flip-flops E and F
 - ↘
 - 4-bit binary up-counter $A = 0bA_3A_2A_1A_0$
 - Active-low reset signal $reset_b$ puts us in state S_idle , where we remain while signal $Start = 0$ clr-A-F
 - Status signals
 - $Start = 1$ initiates the system's operation by clearing A and F . At each subsequent clock pulse, the counter is incremented by 1 until the operations stop. incr-A
 - Control signals in blue.
 - Bits A_2 and A_3 determine the sequence of operations:
 - If $A_2 = 0$, set E to 0 and the count continues clr-E
 - If $A_2 = 1$, set E to 1; additionally, if $A_3 = 0$, the count continues, otherwise, wait one clock pulse to set F to 1 and stop counting (i.e., back to S_idle) set-E set-F
- When does counting stop? $A = ?$ (101)

Design Example #1

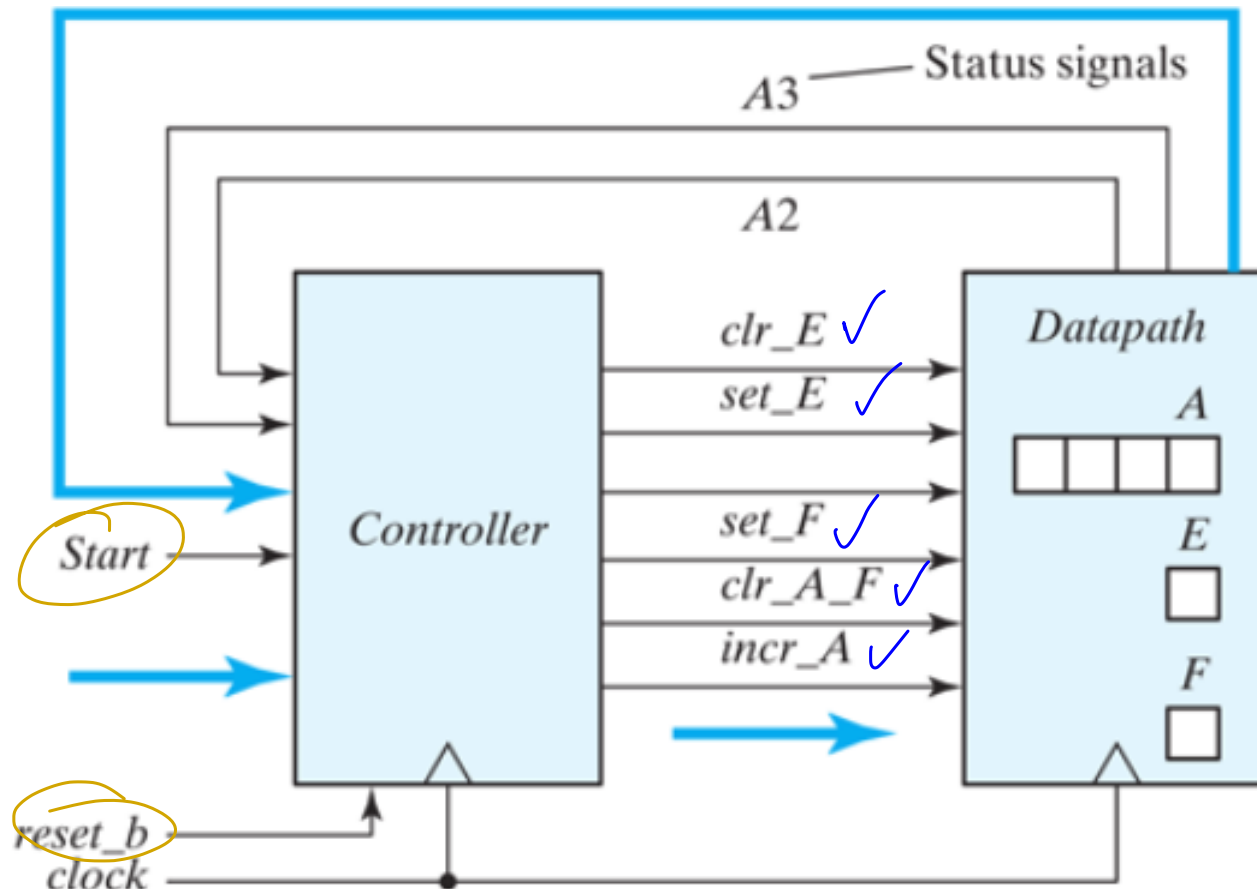- ❖ The system can be represented by the following block diagram:



Design Example #1 (ASM → ASMD Chart)

❖ Synchronous or asynchronous reset?

