

EE/CSE 371
Design of Digital Circuits and Systems

Lecture 4: Memory II

Lab 2 Notes

- ❖ Implementing a few **RAM variants** on the DE1-SoC
 - Using both a library catalog and user-specified RAM modules
- ❖ Learn how to create and use a **memory initialization file (.mif)** to initialize memory on your board
- ❖ Feel free to reuse other modules (*e.g.*, input, clock divider, 7-seg, counter) from 271/369
 - Simple modules don't need diagrams or simulations, but they should be shown in the block diagram and mentioned in your report

Memory Type #2: RAM

- ❖ Random-Access Memory
 - Can read and write to any address instead of having to read in sequence (*e.g.*, a magnetic disk)
- ❖ Can be implemented using different semiconductor technologies:
 - Static RAM (SRAM): uses flip-flops to store data
 - Dynamic RAM (DRAM): uses capacitors and transistors to store data that need to be periodically refreshed
 - SRAM is faster but more expensive than DRAM
- ❖ In a typical home computer:
 - CPU registers and caches are SRAM
 - “Memory” is *synchronous* DRAM (SDRAM)

Example RAM Hardware

- Internal structure of an 8×4 static RAM:
 - Figure 15.18 from Wakerly

2^3 words

3 bits for address.

Write enable


CS_L

output enable

WE_L

OR

IOE_L

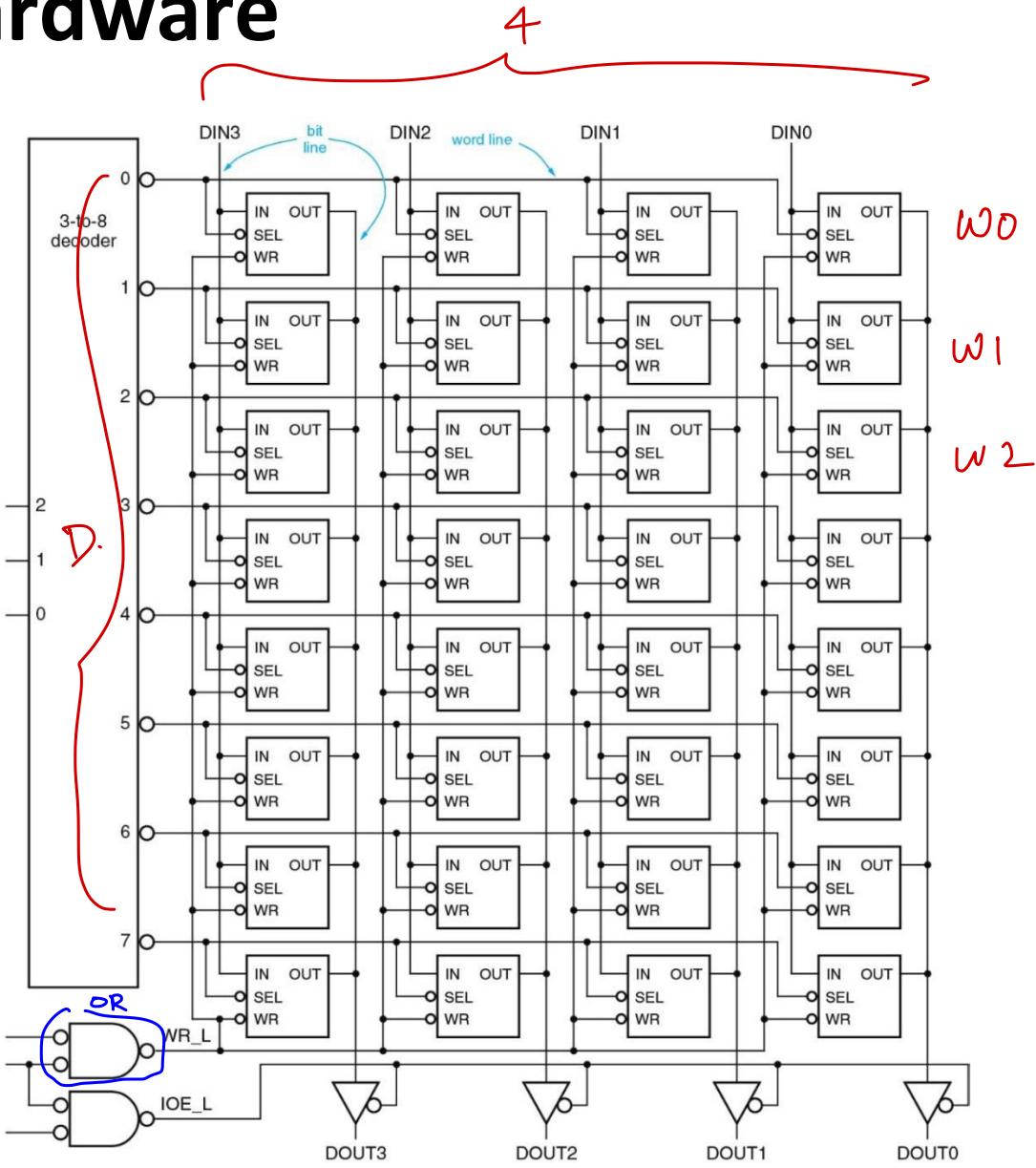

RAM Variants

- ❖ Note that not all of the terminology used here is standardized:

1) Synchronicity

- Are the operations controlled by the clock?
- Can be applied to reading and writing independently

2) Number of ports

- Not in the same sense as number of SV module ports
- Can roughly think of as “channels” (set of addr in, data in, write enable, and data out ports) – how many reads and writes can occur simultaneously?

3) Address independence

- Are the port’s read and write operation based on the same or independent addr in buses?

Synchronous Single-Port RAM (Review)

❖ Synchronous Inputs:


- wren (1 = write, 0 = read)
- addr (A -bit address)
- din (D -bit data)

❖ Synchronous Output:

- dout (D -bit data)

❖ Implementation hints:

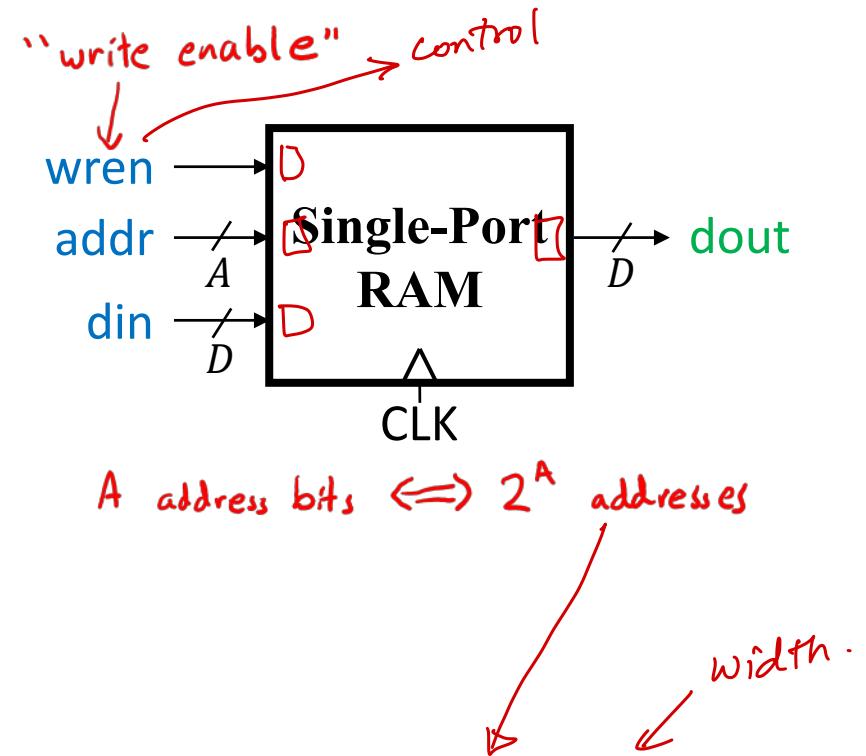- Will need an internal RAM array of what size? $2^A \times D$
- To synchronize, should update on clock triggers $\text{always_ff} @ (\text{posedge clk})$
- What should dout do when wren = 1? also set to din



Synchronous Single-Port RAM (Review)

```
module RAM_single #(parameter A, D)
    (clk, wren, addr, din, dout);

    input logic clk, wren;
    input logic [A-1:0] addr;
    input logic [D-1:0] din;
    output logic [D-1:0] dout;

    logic [D-1:0] RAM [0:2**A-1];
```

*data type
Packed array
width*

*could be either ordering since
we aren't loading from a file*


*Unpacked array
Depth.*

```
always_ff @(posedge clk) begin
    if (wren) begin // write
        RAM[addr] <= din;
        dout <= din;
    end
    else
        // read
        dout <= RAM[addr];
end // always_ff
```

endmodule

Simplified Synchronous Dual-Port RAM

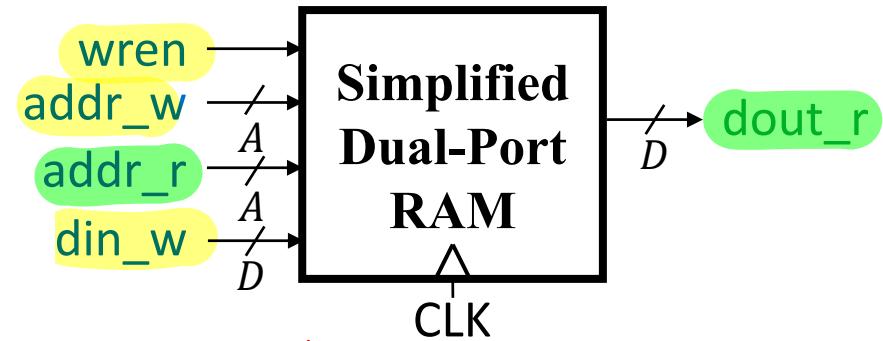- ❖ 2 ports with 1 dedicated to writing and the other dedicated to reading
- ❖ Synchronous Inputs:
 - wren (1 = write, 0 = read)
 - addr_w (A -bit address)
 - addr_r (A -bit address)
 - din_w (D -bit data)
- ❖ Synchronous Output:
 - dout_r (D -bit data)
- ❖ Differences in SystemVerilog?



$$\text{Depth} = 2^A \quad 2^A \times D.$$

Width = D .

$\text{RAM}[\text{addr_w}] \leq \text{din_w};$
 $\Rightarrow \text{dout_r} \leq \text{RAM}[\text{addr_r}];$

Special case
 $\text{addr_w} == \text{addr_r}$
 Pass new value.


Simplified Synchronous Dual-Port RAM (SV)

```
module RAM_dual_simple #(parameter A, D)
    (clk, wren, addr_w, addr_r, din_w, dout_r);

    input logic clk, wren;
    input logic [A-1:0] addr_w, addr_r;
    input logic [D-1:0] din_w;
    output logic [D-1:0] dout_r;


    logic [D-1:0] RAM [0:2**A-1];

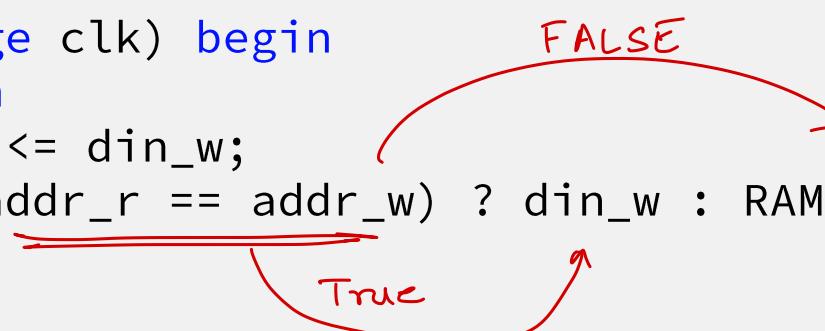    always_ff @(posedge clk) begin
        if (wren) begin
            RAM[addr_w] <= din_w;
            dout_r <= (addr_r == addr_w) ? din_w : RAM[addr_r];
        end
        else
            dout_r <= RAM[addr_r];
    end // always_ff
endmodule
```



Synchronous Dual-Port RAM

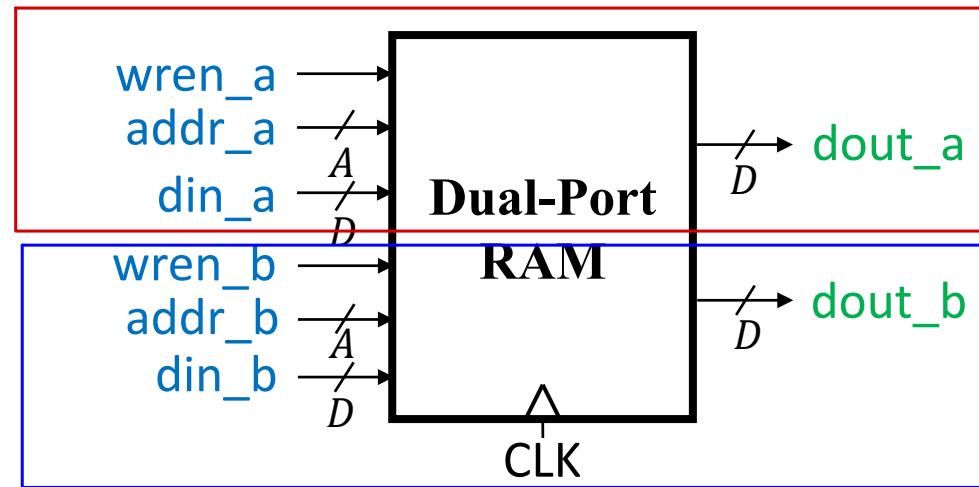- ❖ The most general configuration – each port can either read or write
- ❖ Synchronous Inputs:
 - wren_a and wren_b
 - addr_a and addr_b
 - din_a and din_b
- ❖ Synchronous Output:
 - dout_a and dout_b
- ❖ Differences in SystemVerilog?



2 Copies of Single port RAM.

Special case: When $addr_a/b$ Conflict especially when writing.



Solution! Assign priority to one of the ports.
design decision →

Memory

- ❖ Several forms of memory are available, which include:
 - ~~Secondary memory (e.g., hard disk, flash drive)~~
 - Read-only memory (ROM)
 - Random-access memory (RAM)
 - Register files
 - Small, fast, fixed-sized memory that hold CPU data state
 - First in, first out (FIFO) buffers

Memory Type #3: Register File

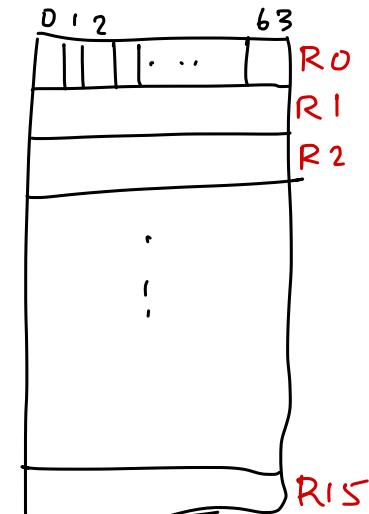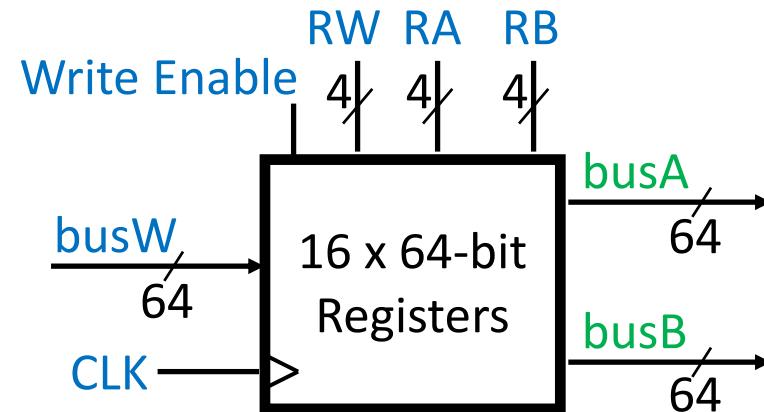- ❖ Register File – a collection of registers
 - 1 input data port – can only write to 1 register at a time
 - 1+ output data ports – can read from 1+ register at a time
 - Address inputs to specify read/write targets
 - Write enable
- ❖ Frequently used in CPUs or as fast buffers
- ❖ Example:



ARM




instruction set.

ADD R0, R1, R2 ;

Assembly
Language .

$$R0 = R1 + R2$$

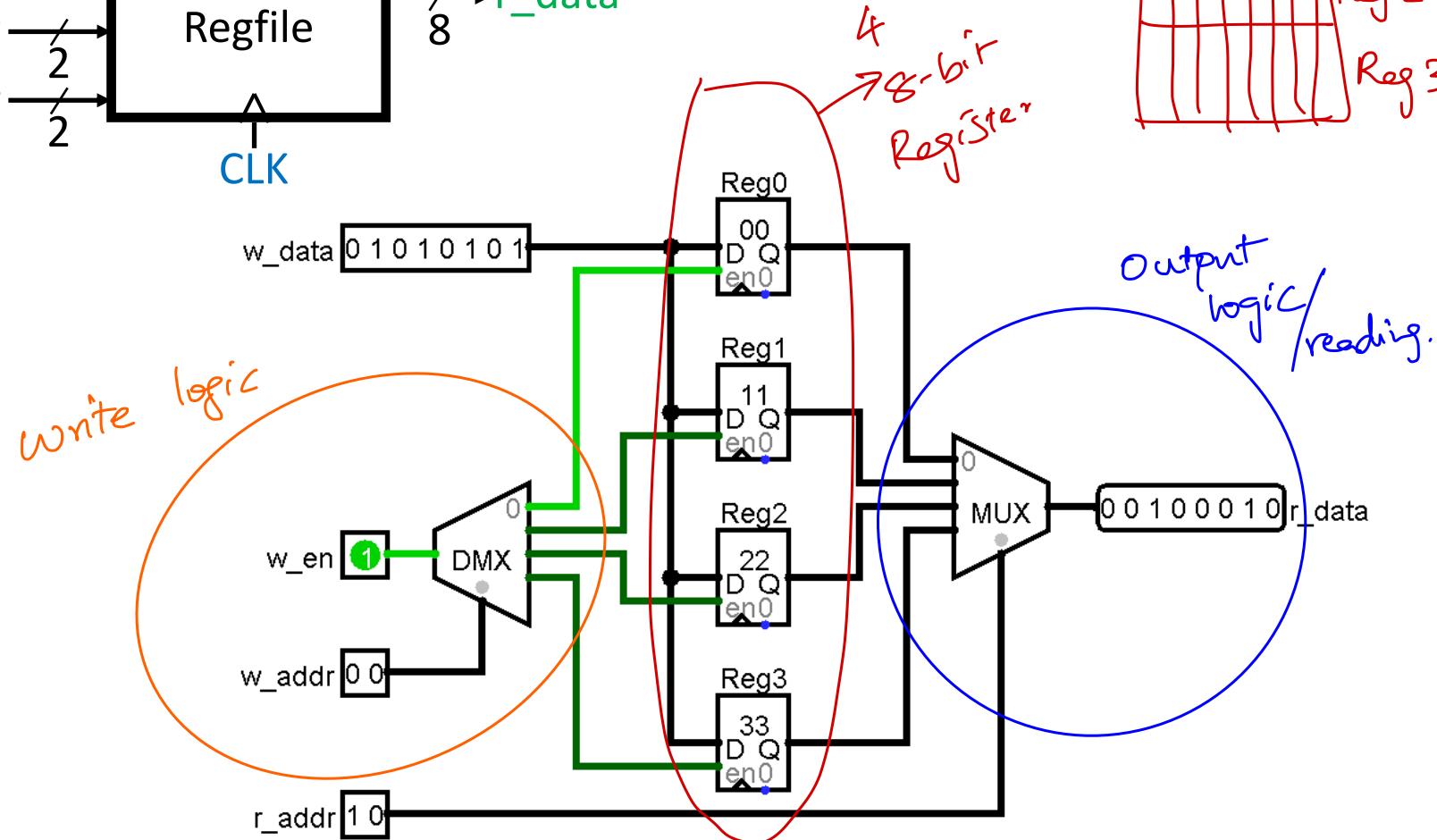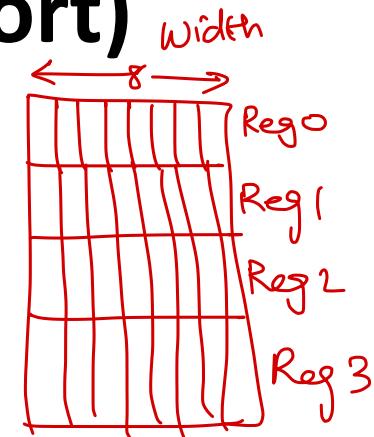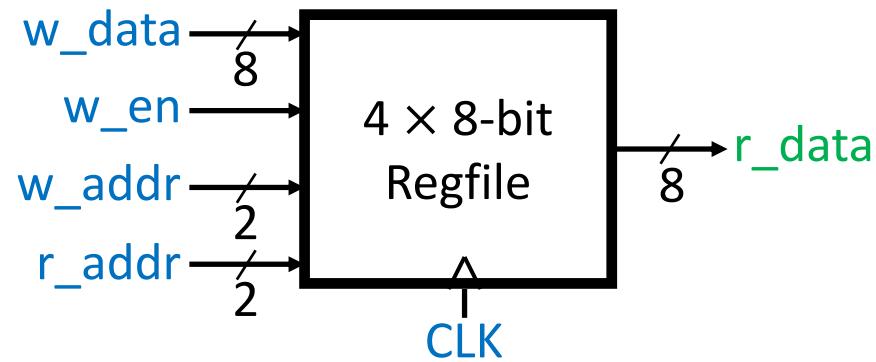Simple Register File (4 reg, 1 read port)



Memory Review

- ❖ Can think of reg file as a 2-D array of D flip-flops:

Logic [7:0] Reg-file [0:3];

- ❖ The simple reg file was labeled 4×8

- SystemVerilog array declaration:

→ Data width.
(W)

- ❖ For a generic reg file with parameters D_WIDTH and A_WIDTH:

- Depth: $2^{*\# \text{ of Address bits}}$

Address width
(# of Address bits)

- Width: D_WIDTH.

- SystemVerilog array declaration:

Logic [D_width-1:0] Gen-Reg-File [0: 2** A_Width - 1];

Register File with 1 Read Port (SV)

4x8
Reg File .

```
module reg_file #(parameter D_WIDTH=8, A_WIDTH=2)
    (clk, w_data, w_en, w_addr, r_addr, r_data);

    input logic clk, w_en;
    input logic [A_WIDTH-1:0] w_addr, r_addr;
    input logic [D_WIDTH-1:0] w_data;
    output logic [D_WIDTH-1:0] r_data;

    // array declaration (registers)
    logic [D_WIDTH-1:0] array_reg [0:2**A_WIDTH-1];

    // write operation (synchronous)
    always_ff @(posedge clk)
        if (w_en)
            array_reg[w_addr] <= w_data;

    // read operation (asynchronous)
    assign r_data = array_reg[r_addr];

endmodule
```

Where's the Hardware?

```
module reg_file #(parameter D_WIDTH=8, A_WIDTH=2)
    (clk, w_data, w_en, w_addr, r_addr, r_data);

    input logic clk, w_en;
    input logic [A_WIDTH-1:0] w_addr, r_addr;
    input logic [D_WIDTH-1:0] w_data;
    output logic [D_WIDTH-1:0] r_data;

    // array declaration (registers)
    logic [D_WIDTH-1:0] array_reg [0:2**A_WIDTH-1];

    // write operation (synchronous)
    always_ff @(posedge clk)
        if (w_en)
            array_reg[w_addr] <= w_data;

    // read operation (asynchronous)
    assign r_data = array_reg[r_addr];
endmodule
```



Registers

Write logic (Demux).

r-addr.

Output logic.

Register File with 2 Read Ports

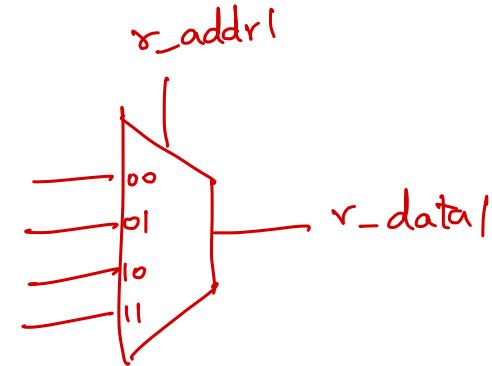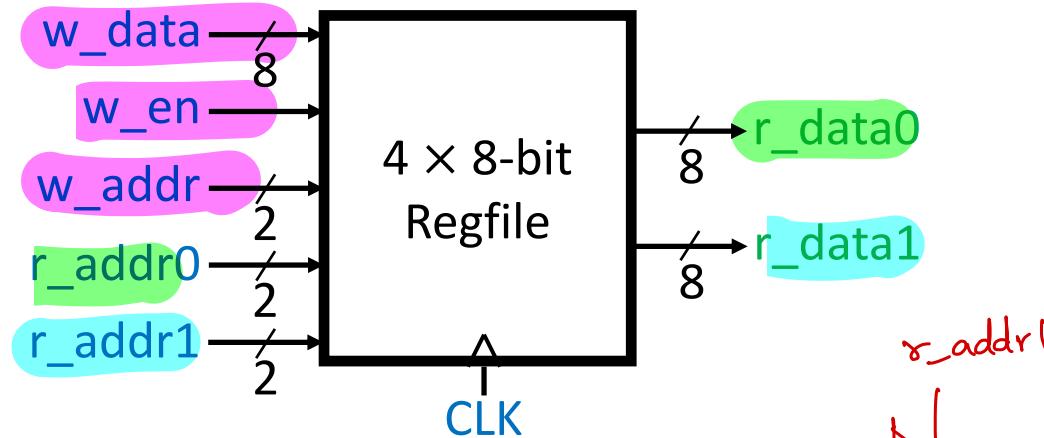

- ❖ What would change in hardware?

Add mux

- ❖ What would change in SystemVerilog?

Add
assign
to previous
SV.


```
assign r_data1 = array_reg[r_addr1];
```

Register File with Synchronous Read

- ❖ Back to the 1 read port version, but now we want to make reading *synchronous*:
 - What would change in SystemVerilog?

always_ff @ (posedge CLK)
r_data <= array-reg [r_addr];

- What would change in hardware?

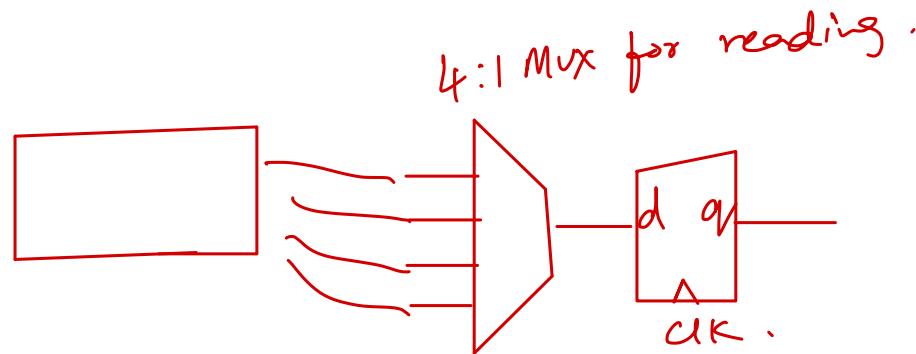


Technology Break

Memory Type #4: FIFO Buffer

❖ First-In First-Out (FIFO) Buffer

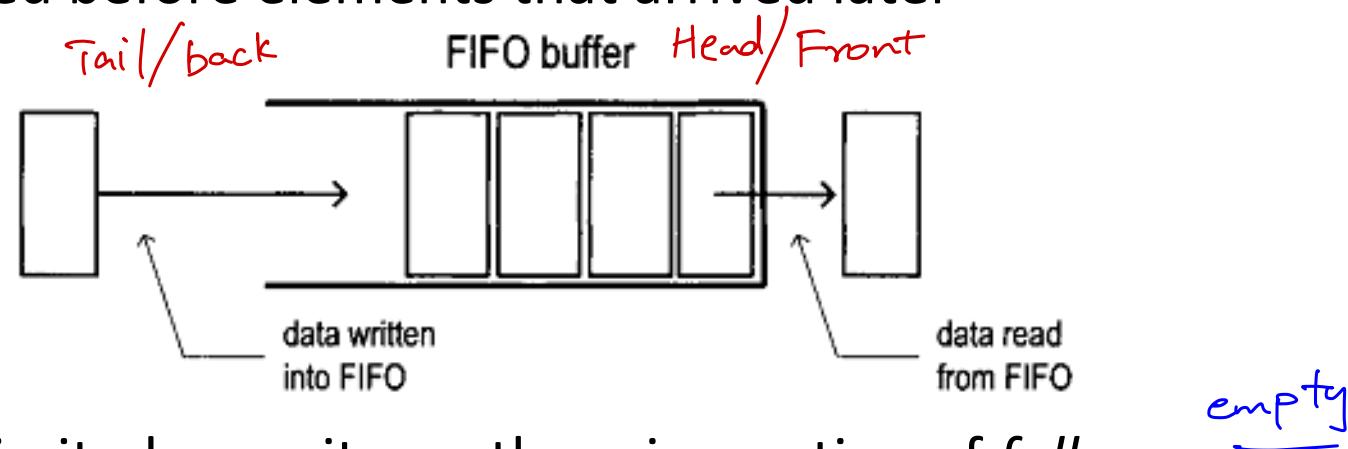
- Data storage such that elements that arrived earlier are accessed before elements that arrived later



- Has a limited capacity, so there is a notion of *fullness*
- Useful for synchronization, especially in communication (e.g., UART, disk, network)

FIFO Buffer Functionality

- ❖ Implementation we will work towards:

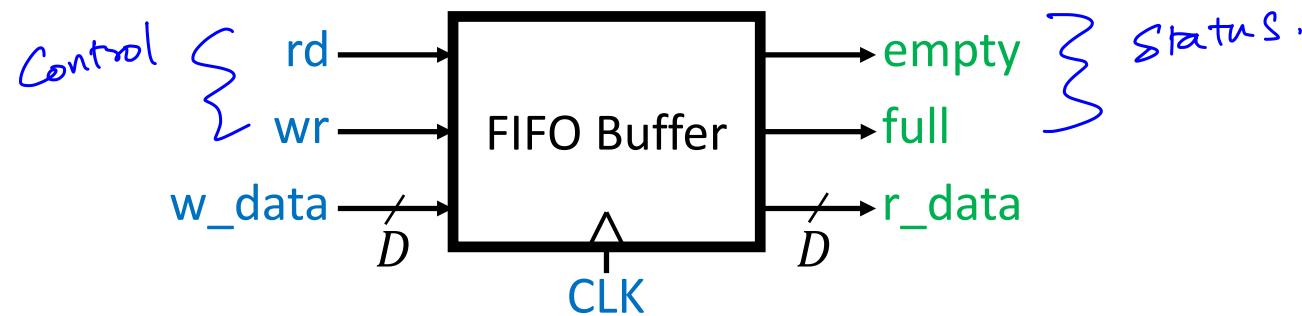


- **rd** signals to read the next element on **r_data**,
wr signals to write **w_data** into the buffer
- Outgoing data is read from the *front/head* of the buffer and incoming data is written to the *back/tail* of the buffer
- Can be implemented by wrapping a regular memory component with a special *controller*
 - However, the FIFO buffer has no visible notion of address!

FIFO Read Configurations

- ❖ First Word Fall Through (FWFT)
 - *Asynchronous* read: front element of buffer always “falls through” and is immediately available on the output bus
 - Including when an element is written to an empty buffer!
 - rd therefore acts more like a “remove” signal
- ❖ Standard
 - *Synchronous* read: front element of buffer becomes available on next clock cycle after rd is asserted
 - rd therefore acts more like a “request” signal


FIFO Read Configurations

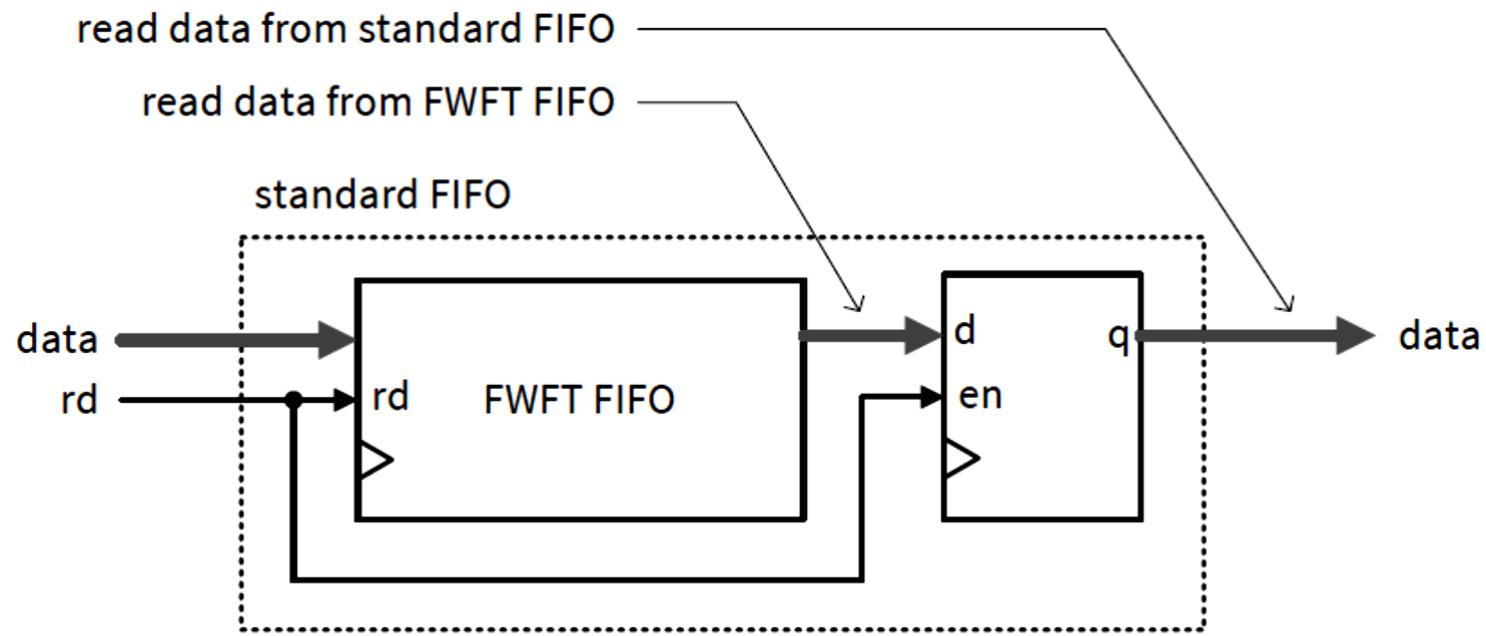- ❖ Read configuration comparison
 - FWFT can be converted to standard by registering the output:




FIFO Implementation


- ❖ A FIFO buffer is often implemented as a *circular queue* with two pointers:
 - **rd_ptr** indicates the location of the front/head (*i.e.*, the first valid data) and advances when rd is asserted
 - **wr_ptr** indicates the location of the back/tail (*i.e.*, the first empty element) and advances when wr is asserted
 - empty and full as buffer fullness status indicators
 - These are tricky because both situations have $\text{rd_ptr} == \text{wr_ptr}$

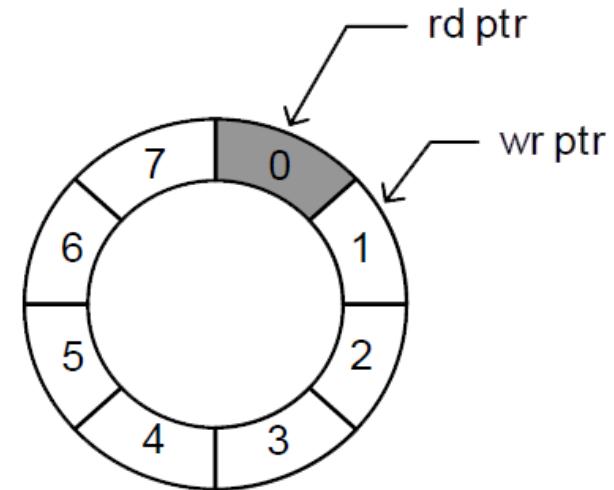


Circular Queue Example Operation

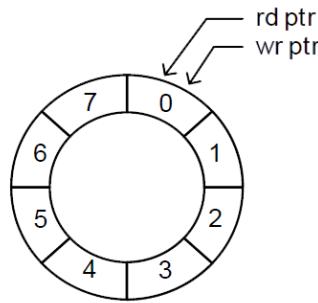


(a). initial (empty)

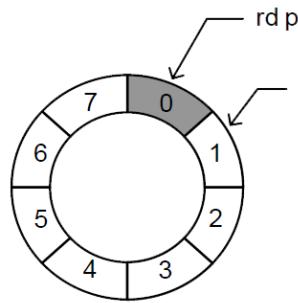


(b). after a write

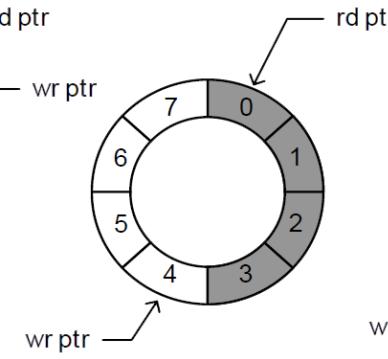


(c). 3 more writes

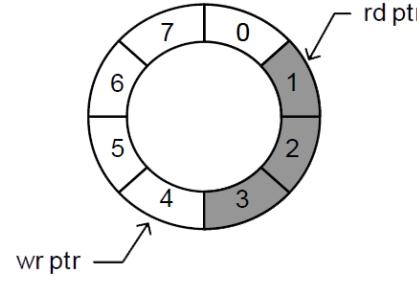


(d). after a read

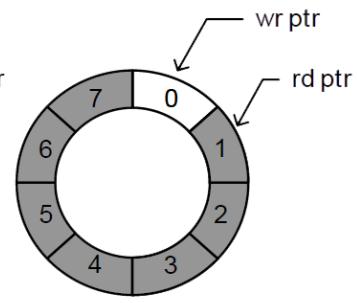


(e). 4 more writes

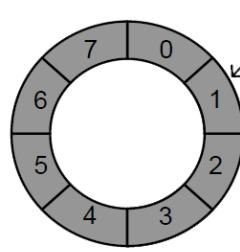


(f). 1 more write (full)

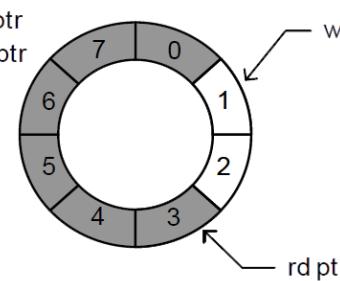

(g). 2 reads

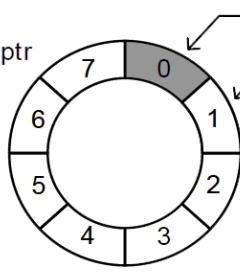


(h). 5 more reads

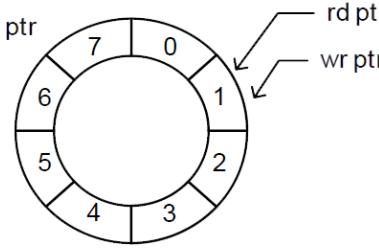

(i). 1 more read (empty)

Circular Queue Implementation

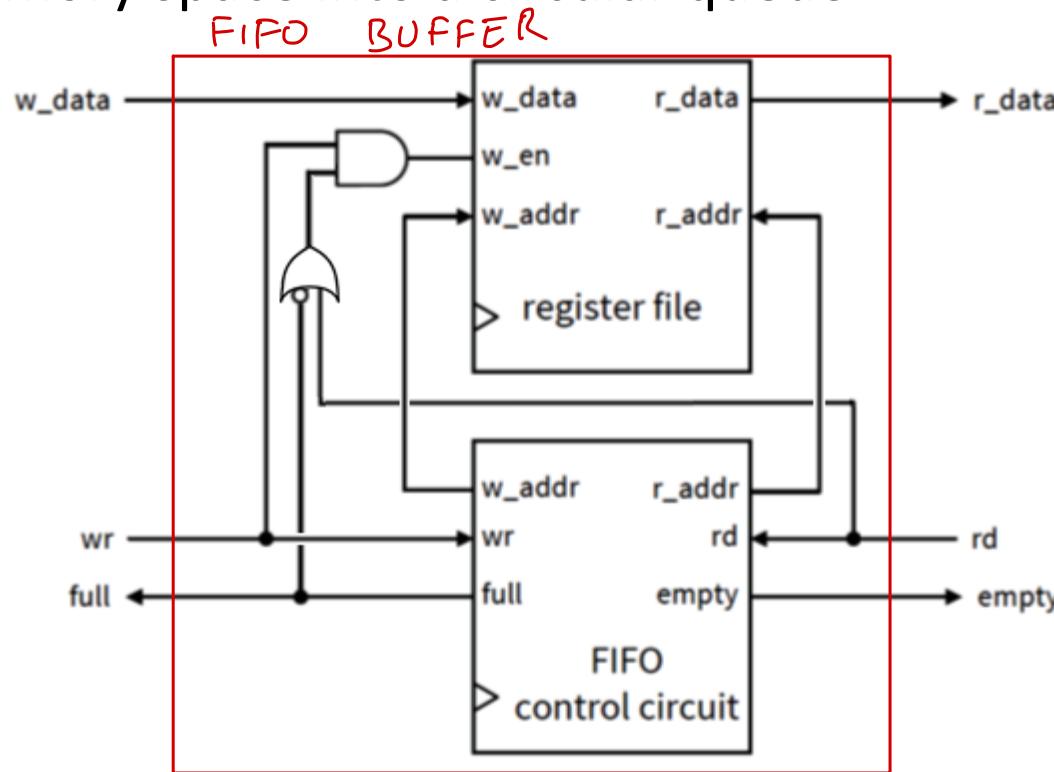- ❖ A circular queue can be implemented using a RAM module and a *FIFO controller*
 - The controller handles the “arrangement” of the linear memory space into a circular queue



FIFO Controller

- ❖ FIFO controller internals: UP ✓

- rd_ptr and wr_ptr are *counters*
- empty and full are *flip-flops*
- Next state logic based on inputs rd and wr:

rd	wr	rd_ptr	wr_ptr	empty	full
0	0	—	—	—	—
0	1	—	if(\neg full) +1	0	if(\neg full) \neg rd_ptr-next == wr_ptr-next
1	0	if(\neg empty) +1	—	if(\neg empty) rd_ptr-next == wr_ptr-next	0
1	1	+1	+1	—	—

FIFO Controller

- ❖ FIFO controller internals:

- rd_ptr and wr_ptr are *counters*
- empty and full are *flip-flops*
- Next state logic based on inputs rd and wr:
 $\begin{matrix} \text{R} \\ \text{W} \end{matrix}$
 - 00 → no change
 - 11 → advance both rd_ptr and wr_ptr
full and empty don't change
 - 10 → if not empty: advance rd_ptr,
set full = 0,
set empty = 1 if rd_ptr == wr_ptr
 - 01 → if not full: advance wr_ptr,
set empty = 0,
set full = 1 if rd_ptr == wr_ptr

FIFO Controller (SV, 1/3)

```
module fifo_ctrl #(parameter A_WIDTH=4)
    (clk, reset, rd, wr, empty, full, w_addr, r_addr);

    input logic clk, reset, rd, wr;
    output logic empty, full;
    output logic [A_WIDTH-1:0] w_addr, r_addr;

    // next state signal declarations ✓ PS ns
    logic [A_WIDTH-1:0] rd_ptr, rd_ptr_next;
    logic [A_WIDTH-1:0] wr_ptr, wr_ptr_next;✓
    logic empty_next, full_next;
    ✓ ✓

    // output assignments
    assign w_addr = wr_ptr;
    assign r_addr = rd_ptr;

    // [continued on next slide...]
```

FIFO Controller (SV, 2/3)

```
// fifo controller logic
always_ff @(posedge clk) begin
    if (reset)
        begin
            wr_ptr <= 0;
            rd_ptr <= 0;
            full    <= 0;
            empty   <= 1;
        end
    else
        begin
            wr_ptr <= wr_ptr_next;
            rd_ptr <= rd_ptr_next;
            full    <= full_next;
            empty   <= empty_next;
        end
// [continued on next slide...]
```

FIFO Controller (SV, 3/3)

```
// next state logic
always_comb begin
    // default: keep current values
    rd_ptr_next = rd_ptr;
    wr_ptr_next = wr_ptr;
    empty_next = empty;
    full_next = full;

    // [continued in next box...]
```

```
        case ({rd, wr})
            2'b11: // read and write
                begin
                    rd_ptr_next = rd_ptr + 1'b1;
                    wr_ptr_next = wr_ptr + 1'b1;
                end
            2'b10: // read
                if (~empty) begin
                    rd_ptr_next = rd_ptr + 1'b1;
                    if (rd_ptr_next == wr_ptr)
                        empty_next = 1;
                    full_next = 0;
                end
            2'b01: // write
                if (~full) begin
                    wr_ptr_next = wr_ptr + 1'b1;
                    empty_next = 0;
                    if (wr_ptr_next == rd_ptr)
                        full_next = 1;
                end
            2'b00: ; // no change
        endcase
    end // always_comb
endmodule
```

FIFO Buffer (SV)

Top level

```
module fifo #(parameter D_WIDTH=8, A_WIDTH=4)
    (clk, reset, rd, wr, empty, full, w_data, r_data);

    input logic clk, reset, rd, wr;
    output logic empty, full;
    input logic [D_WIDTH-1:0] w_data;
    output logic [D_WIDTH-1:0] r_data;

    // signal declarations
    logic [A_WIDTH-1:0] w_addr, r_addr;
    logic w_en;

    // enable write only when FIFO is not full
    assign w_en = wr & (~full | rd);

    // instantiate FIFO controller and register file
    fifo_ctrl #(A_WIDTH) control (*.*);
    reg_file #(D_WIDTH, A_WIDTH) mem (*.*);

endmodule
```

Memory Controllers

- ❖ A *memory controller* is an interface circuit between user logic and the physical memory device
 - Abstracts away details of physical memory device while providing a consistent interface to the user
 - The FIFO controller we just discussed allows a user to interface with the register file we implemented on the FPGA's internal memory module
- ❖ Memory controllers are found with all kinds of memory
 - Your DE1-SoC contains memory controllers for SDRAM and DDR3 (and controllers for a bunch of other things like USB, VGA, PS/2, I2C)

DE1-SoC Memory Revisited


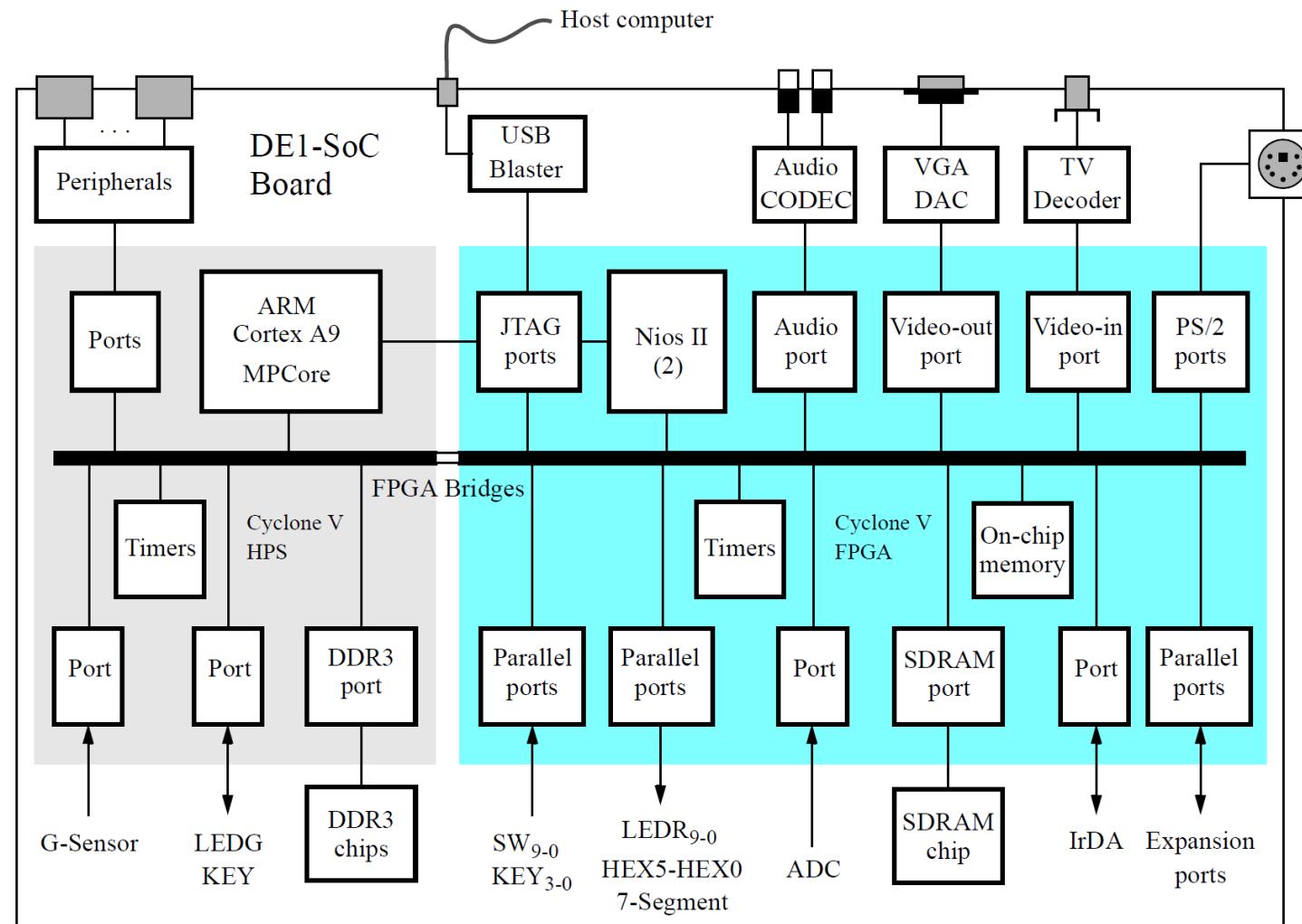


Figure 1. Block diagram of the DE1-SoC Computer.

SDRAM Controller

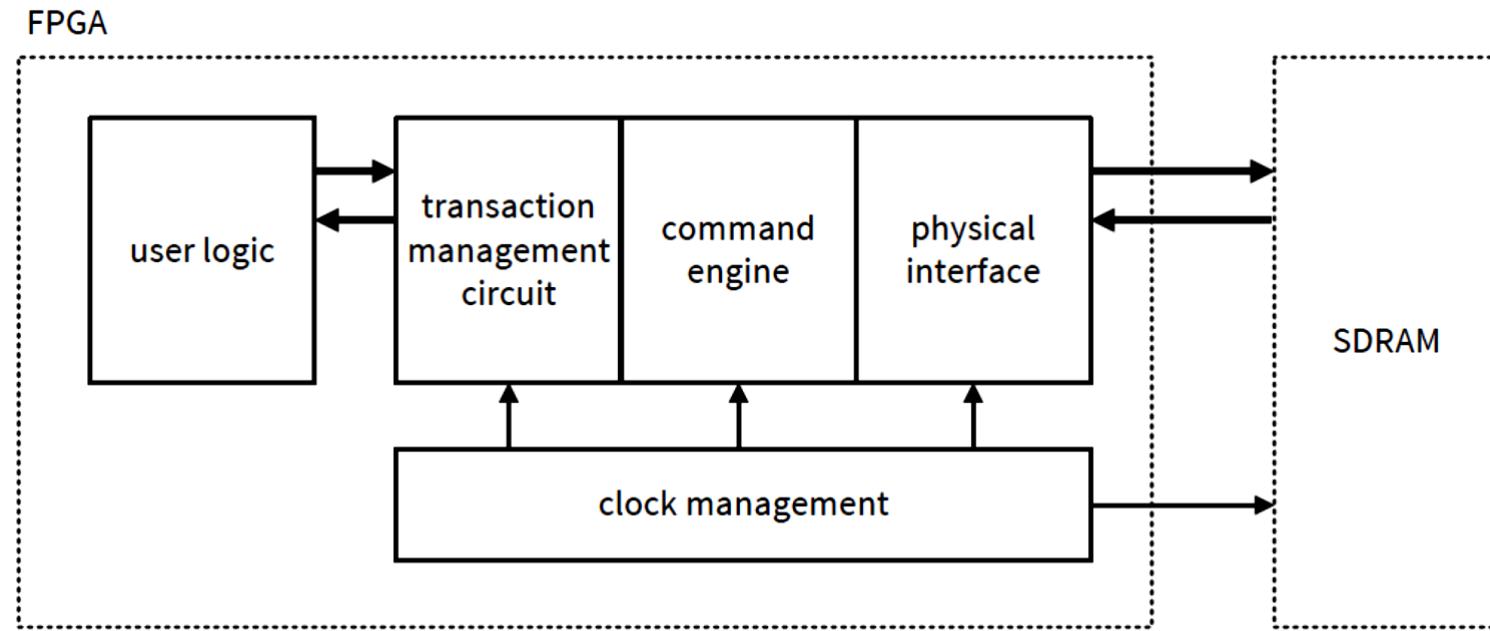

- ❖ High-performance controllers are very complex!
 - Design depends on individual FPGA and SDRAM devices
 - Usually constructed with vendor-supplied IP core