

Ternary Operator


Output =

❖ Conditional assignment

■ `select ? <if_expr> : <else_expr>`

- If `select` is true, then evaluates to `<if_expr>`, otherwise evaluates to `<else_expr>`


■ What does this look like in hardware?

 

❖ Example: tristate buffer

■ `enable ? in : 'bZ`

 - When enabled, pass the input to the output, otherwise be high impedance



enable	A	B
0	0	Z
0	1	Z
1	0	0
1	1	1

$B = \text{enable} ? A : 'bZ$

✓

Bit Manipulation

❖ Concatenation: $\{sig, ..., sig\}$

- Ordering matters; result will have combined widths of all signals

❖ Replication operator: $\{n\{m\}\}$

- repeats value m, n times

$\{2\{1\}\}$

❖ Exercise: arithmetic right shift preserves the sign bit

```
logic [7:0] x = <some 8-bit constant>;
// replicate the behavior of y = x >>> 3
assign y = { {3{x[7]}}, x[7:3] };
```

$b_7 \ b_6 \ b_5 \ \dots \ b_1 \ b_0$ $b_7 = 0$

$y = 1111 \ b_6 \ b_5 \ b_4 \ b_3$

$y = 0000 \ b_6 \ b_5 \ b_4 \ b_3$

“Looping”

- ❖ Code is compiled to hardware, so no execution
 - “Loops” must be *statically unrolled* into multiple statements
 - Loops are just for convenience in code writing
- ❖ `repeat (#) <statement(s)>`
 - Makes # copies of statement(s)
- ❖ `for (i=0; i<#; i++) <statement(s)>`
 - Makes # copies of statement(s) that vary based on i
- ❖ `generate` (see reference docs)
 - More “powerful” for-loop typically used for:
 - 1) Module instantiation
 - 2) Changing the structure of parameterized modules
 - 3) Functional and formal verification using assertions

Modules

- ❖ “Black boxes” that we define and instantiate that form the basic building blocks of our design hierarchy
 - **Ports** form the connections between a module and its environment
 - Ports have directionality (*input*, *output*, *inout*), which can be declared within the module or within the port list

```
module tristate(out, in, enable);  
  input logic in, enable;  
  output tri out;  
  
  assign out = enable ? in : 'Z;  
endmodule
```

C-style

```
module tristate(output tri out,  
               input logic in,  
               input logic enable);  
  assign out = enable ? in : 'Z;  
endmodule
```

Module Instantiation

- ❖ Name an instance and define its port connections

- `<type> <name> (<port connections>);`

- ❖ Assume we have: `logic in, enable; tri out;`

1) Positional connections:

```
// must follow defined port ordering  
// signal names can be anything  
tristate my_tri(out, in, enable);
```

2) Named/explicit connections:

```
// any ordering & names allowed  
tristate my_tri(.out(out), .in(in), .enable(enable));
```

3) *.name* implicit connection:

```
// signal and port names must match exactly  
tristate my_tri(.out, .in, .enable);
```



Parameters

- ❖ A **parameter** is a named constant

- Typically used for widths and timing

```
parameter N = 8;           // bus width
parameter period = 100;    // timing constant
```

- ❖ A parameterized module:


- `module <name> #(<parameter list>) (<port list>);`
- Parameters should be given default values
 - e.g., `#(parameter N = 8)`

- ❖ Exercises:

- Define a parameterized tristate (tristate buffer)
- Define a parameterized multibitAND

Lab 1 Notes

 - ❖ Read the spec carefully!
 - For scenarios that are not described, it's up for you to define; describe and defend your decisions in your report
 - Also read *371_Assignments.pdf*
- ❖ Plan and design *before* you start coding!
- ❖ Test your code in small pieces *as you go*
 - Lab report due before your demo
 - Short sessions (3 min) on LabsLand



EE/CSE 371

Design of Digital Circuits and Systems

Lecture 2: Finite State Machine Review

Relevant Course Information

1. HW 1 and Lab 1 due this week

Homework can be completed in groups of up to 4
Labs can be completed in groups of up to 2

2. Make sure LabsLand is setup and synthesized beforehand

Parameters (Review)

- ❖ A **parameter** is a named constant

- Typically used for widths and timing

```
parameter N = 8;           // bus width  
parameter period = 100;    // timing constant
```

- ❖ A parameterized module:

- `module <name> #(<parameter list>) (<port list>);`
- Parameters should be given default values
 - e.g., `#(parameter N = 8)`


Review Question

Concatenation: $\{ sig, sig \dots \}$

Replication: $\{ n \{ m \} \}$

Ternary: $out = enable ? in : b'z;$

 - ❖ There are two forms of bit extensions: **zero-extension** (add 0s) and **sign-extension** (copy MSB)
- ❖ Write out SystemVerilog pseudocode for a parameterized **extender** module $M=4, N=8$
 - Inputs `sign` (1 bit), `in` (M bits); output `out` (N bits $> M$)
 - `out` should either be the sign-extended version of `in` (`sign` = 1) or the zero-extended version of `in` (`sign` = 0)




```

module extender #(parameter M = 4, N = 8)
    (output [N-1:0] out,
     input [M-1:0] in,
     input sign);
    assign out = sign ? {{(N-M){in[M-1]}},in} : {{(N-M){1'b0}},in};
endmodule

```

Handwritten annotations: A red arrow points from the `in[M-1]` expression to the text "MSB of in". A blue arrow points from the `sign` variable to the conditional operator `?`.

❖ Hardware if $M = 4$ and $N = 8$:

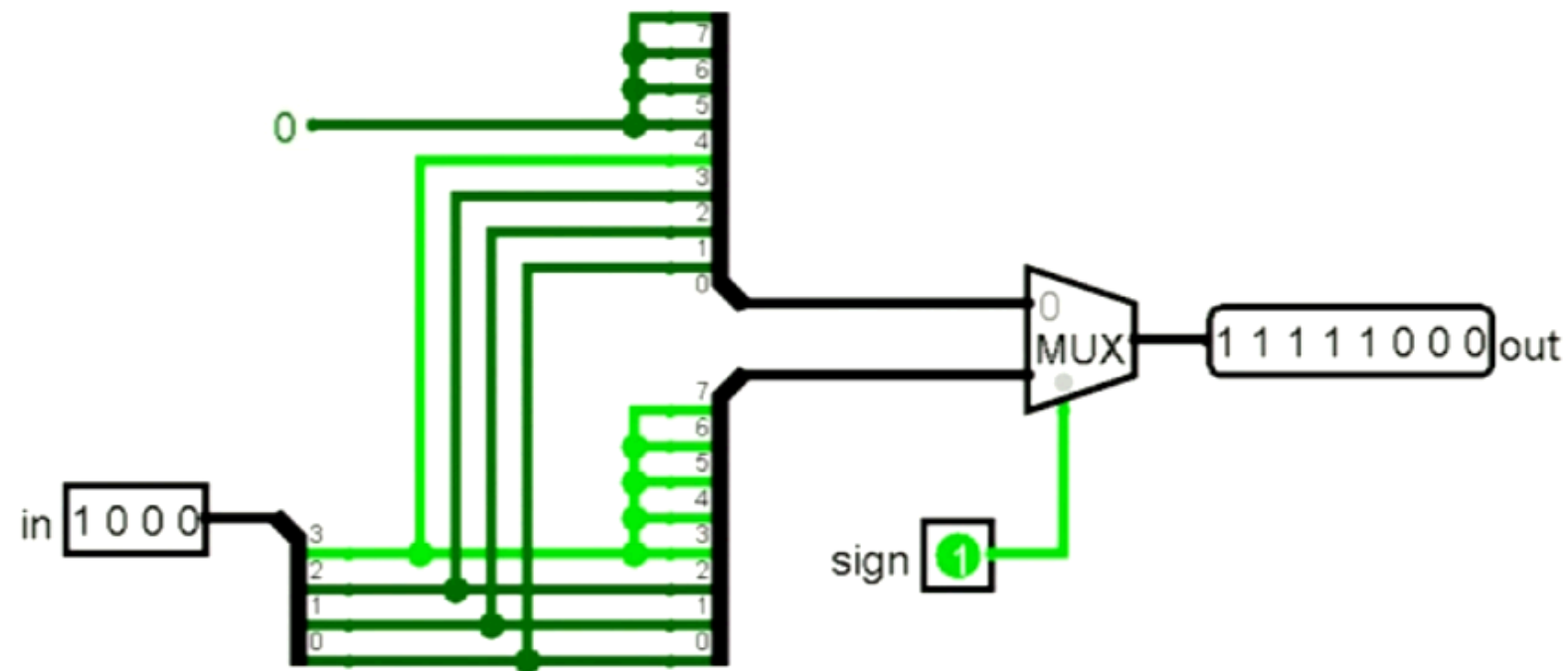

Lecture Outline

- ❖ **SystemVerilog Review & Tips (Cont.)**
- ❖ FSMs
- ❖ Testbenches

Structural vs. Behavioral Revisited

- ❖ Not a strict definition of these terms, so exact classification is not that important
- ❖ Structural:
 - Instantiating modules (library and user-defined) and defining port connections
 - `assign`: continuous assignment
 - Used with nets

Verilog Procedural Blocks

- ❖ A *procedural block* is made up of behavioral code in the form of procedural statements that are executed sequentially
 - The block itself is awakened/triggered in a non-sequential manner
- ❖ `initial`: block triggered once at time zero
 - Non-synthesizable (*i.e.*, for simulation/testbenches only)
- ❖ `always`: block triggered by a *sensitivity list*
 - Any object that is assigned a value in an `always` statement must be declared as a variable (*e.g.*, `logic` or `reg`).

SystemVerilog Procedural Blocks

- ❖ SystemVerilog introduced variants on always that are generally more robust and more specialized
- ❖ `always_comb`: intended for combinational logic
 - Sensitivity list is automatically built
- ❖ `always_latch`: intended for latch-based logic
 - Sensitivity list is automatically built
- ❖ `always_ff`: intended for sequential logic (*i.e.*, synchronous/clocked)
 - Sensitivity list must be specified

Latch vs. Flip-Flop

- ❖ Both are bistable multivibrators (2 stable states) that can store information

semi-synchronous

q can change when CLK = 1





- ❖ A latch is *asynchronous*; a flip-flop is edge-triggered

```
module my_latch(input logic clk,
               input logic [3:0] d,
               output logic [3:0] q);
```

```
    always_latch
        if (clk) q <= d;
        else q <= q;
endmodule
```

$@(clk, d)$

  


```
module my_ff(input logic clk,
             input logic [3:0] d,
             output logic [3:0] q);
```

```
    always_ff @(posedge clk)
        q <= d;
```


```
endmodule
```

Inferred Latches

 - ❖ **Warning:** easy to write code with inadvertent latches
 - Check your synthesis output for “Inferred latch”
 - Usually from *incomplete assignments* – unspecified branch infers latch behavior
- ❖ **Question:** which of the following will synthesize and, if so, what will the hardware look like?



 
- Demo: Tools → “Netlist Viewers” → “RTL Viewer”



d



clk

 

$\frac{q_{\text{latch}}}{\text{clk}} = 1$

$\frac{q_{\text{ff}}}{\text{pos.}}$

case Statement

❖ Create combinational logic and is easier to read than lots of `if/else` statements

- Must always be inside an `always` block
- Each case has an implied C-style break

```
module seven_seg(bcd, segs);  
    input  logic [3:0] bcd;  
    output logic [6:0] segs;  
  
    always_comb  
        case (bcd)  
            //                abc_defg  
            0: segs = 7'b011_1111;  
            1: segs = 7'b000_0110;  
            2: segs = 7'b101_1011;  
            3: segs = 7'b100_1111;  
            4: segs = 7'b110_0110;  
            5: segs = 7'b110_1101;  
            6: segs = 7'b111_1101;  
            7: segs = 7'b000_0111;  
            8: segs = 7'b111_1111;  
            9: segs = 7'b110_1111;  
  
        endcase  
  
    endmodule
```

case Statement

- ❖ Create combinational logic and is easier to read than lots of `if/else` statements
 - Must always be inside an `always` block
 - Each case has an implied C-style break
 - Remember to use `default` to avoid incomplete assignments!

```
module seven_seg(bcd, segs);  
  
    input  logic [3:0] bcd;  
    output logic [6:0] segs;  
  
    always_comb  
        case (bcd)  
            //                                abc_defg  
            0: segs = 7'b011_1111;  
            1: segs = 7'b000_0110;  
            2: segs = 7'b101_1011;  
            3: segs = 7'b100_1111;  
            4: segs = 7'b110_0110;  
            5: segs = 7'b110_1101;  
            6: segs = 7'b111_1101;  
            7: segs = 7'b000_0111;  
            8: segs = 7'b111_1111;  
            9: segs = 7'b110_1111;  
            → default: segs = 7'bX;  
        endcase  
  
endmodule
```


Other SystemVerilog Resources


- ❖ SystemVerilog Language Reference Manual
 - On ~~Canvas~~^{Piazza}, Files → “Reference Material”
 - 586 pages...
- ❖ SystemVerilog articles
 - <https://www.systemverilog.io/>
 - <http://www.verilogpro.com/>
 - <https://www.chipverify.com/systemverilog/systemverilog-tutorial>
- ❖ One style guide for SystemVerilog
 - <https://www.systemverilog.io/styleguide>
 - We won't enforce, but good guidelines

Lecture Outline

- ❖ SystemVerilog Review & Tips (Cont.)
- ❖ **Finite State Machine Design**
- ❖ Testbenches


Finite State Machines (FSMs)

 - ❖ A convenient way to conceptualize computation over time using a *state transition diagram*
 - Consists of a *set of states*, an *initial state*, and a *transition function*
- ❖ FSM implementations come in 3 blocks:
 - State register (SL)
 - Next state logic (CL)
 - Output logic (CL)



Moore FSM.

MEALY FSM

 

FSM Implementation Notes

enum {s0, s1, s2}
ps, ns;

- ❖ States must be assigned a binary encoding
 - More readable by using parameters or an enum
 - Encoding choices can affect logic simplification
- ❖ Reset signal can be synchronous (responds to clk) or asynchronous (responds to reset)
 - Determined by whether or not reset is in sensitivity list
- ❖ State logic (next state logic + state update) can be written as 1 combined block or 2 separate blocks
- ❖ If input is asynchronous, may want to add a two-flip-flop *synchronizer* to deal with metastability

@ (posedge clk)

@ (posedge clk, posedge reset)



FSM SystemVerilog Design Pattern

- ❖ Which, if any, construct(s) would you expect to use for each of the following basic sections of a module that implements an FSM?

enum {A,B,C} ps,ns;

- *// define states and state variables*
 initial assign always_comb always_ff None
- *// next state logic*
 initial *assign* *always_comb* always_ff None
- *// output logic*
 initial *assign* *always_comb* always_ff None
- *// state update logic*
 initial assign always_comb *always_ff* None