

(individual assessment).
Midterm exam on Wednesday Nov. 1.

Open book, open notes, Laptop allowed

No internet access is allowed.

- ASM / ASMD chart - Algorithms to HW.

- FSM's Mealy vs Moore

- ASMD Design process

- Memory (RAM, ROM, Reg. File, Buffer)

4 per round table rest on side tables.

Division Circuit

- ❖ Design a circuit that implements the long-division algorithm:

$$\begin{array}{r} 15 \\ 9 \overline{) 140} \\ \underline{9} \\ 50 \\ \underline{45} \\ 5 \end{array}$$

(a) An example using decimal numbers

$$\begin{array}{r} \text{divisor} \rightarrow 1001 \quad \begin{array}{r} 00001111 \\ 1001 \overline{) 10001100} \\ \underline{1001} \\ 10001 \\ \underline{1001} \\ 10000 \\ \underline{1001} \\ 1110 \\ \underline{1001} \\ 101 \end{array} \begin{array}{l} \leftarrow \text{quotient} \\ \leftarrow \text{dividend} \\ \leftarrow \text{remainder} \end{array} \end{array}$$

(b) Using binary numbers


- ❖ Considerations:

- Main operations? *Subtract, shift, compare*
- Stop condition? *n iterations if both divisor & dividend are n-bits.*

Division Circuit

- ❖ Design a circuit that implements the long-division algorithm:
 - 1) Double the dividend width by appending 0's in front and align the divisor to the leftmost bit of the extended dividend.
 - 2) If the corresponding dividend bits are \geq the divisor, subtract the divisor from the dividend bits and make the corresponding quotient bit 1. Otherwise, keep the original dividend bits and make the quotient bit 0.
 - 3) Append one additional dividend bit to the previous result and shift the divisor to the right one position.
 - 4) Repeat steps 2 and 3 until all dividend bits are used.

Division Circuit

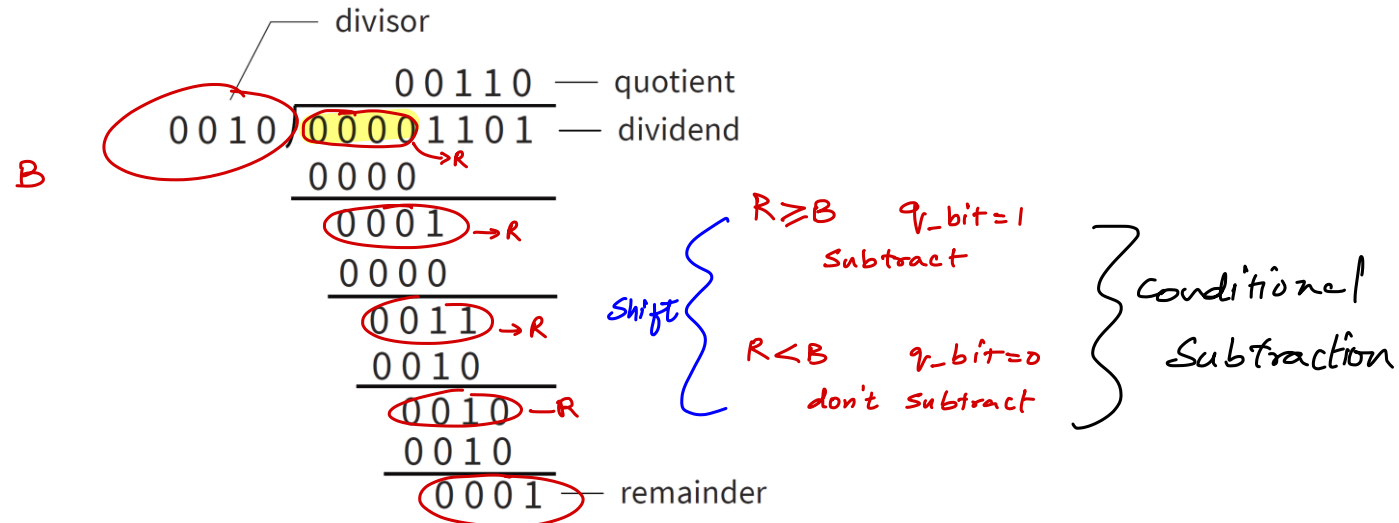

❖ Implementation Notes:

- If current **dividend window** is smaller than the **divisor**, skip subtraction
- Instead of shifting **divisor** to the right, we will shift the **dividend** (and the **quotient**) *to the left*
- We will re-use the lower half of the **dividend** register to store the **quotient**

Expected $Q = 0111$ $R = 0001$


Division Circuit Operation

❖ A few steps of: $q_bit = (R \geq B)$
 $Q_nxt = \{Q[n-2:0], q_bit\}$

$R_tmp = q_bit ? R - B : R$
 $R_nxt = \{R_tmp[n-2:0], Q[n-1]\}$
CL compute

0010 | 1111

DATA PATH

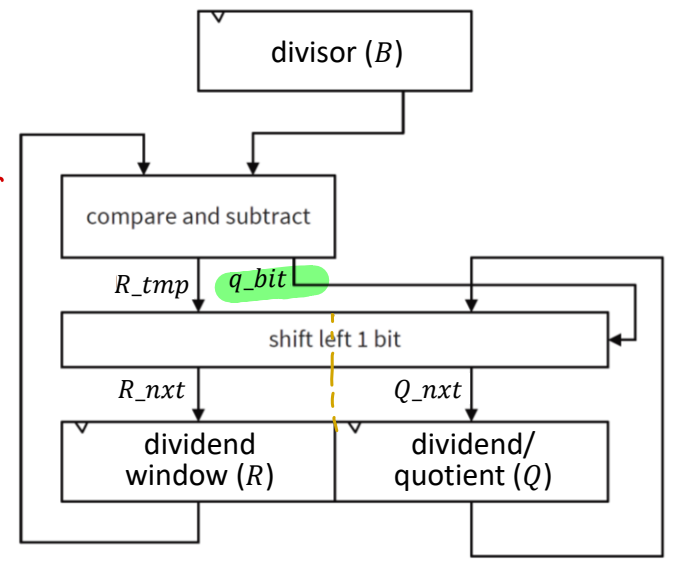

Extended dividend.
dividend.

| Op (done) | B | R | Q | q_bit | R_tmp | R_nxt | Q_nxt | P |
|------------|------|------|------|-------|---------------------|-------|-------|-----|
| Initialize | 0010 | 0000 | 1111 | 0 | 0000 _R | 0001 | 1110 | 100 |
| Compute | 0010 | 0001 | 1110 | 0 | 0001 _R | 0011 | 1100 | 011 |
| Compute | 0010 | 0011 | 1100 | 1 | 0001 _{R-B} | 0011 | 1001 | 010 |
| Compute | 0010 | 0011 | 1001 | 1 | 0001 | 0011 | 0011 | 001 |
| Compute | 0010 | 0011 | 0011 | 1 | 0001 | 0010 | 0111 | 000 |
| Done | 0010 | 0001 | 0111 | X | X | X | X | X |

Division Circuit Specification

❖ Datapath

- $2n$ -bit *register* with bits split into n -bit R and n -bit Q
- Divisor stored in register B , dividend stored in Q , R holds 0
- A “compare and subtract” module outputs $\{R, 0\}$ if $R < B$ and $\{R - B, 1\}$ otherwise ($\{R_tmp, q_bit\}$)
- A *shifter* left shifts q_bit into $\{R_tmp, Q\}$ and outputs to the inputs of R and Q
- A $\lceil \log_2(n + 1) \rceil$ -bit *counter* P

❖ Control

- Inputs Start and Reset, outputs Ready and Done

Decisions

- Status signals: P_zero (all of P)


$R \leftarrow R_tmp$ $R \leftarrow R_next$

Actions


- Control signals: $Load_regs$, $Decr_P$, $Finish_RQ$, $Enable_RQ$

Division Circuit (ASM → ASMD Chart)

State Outline

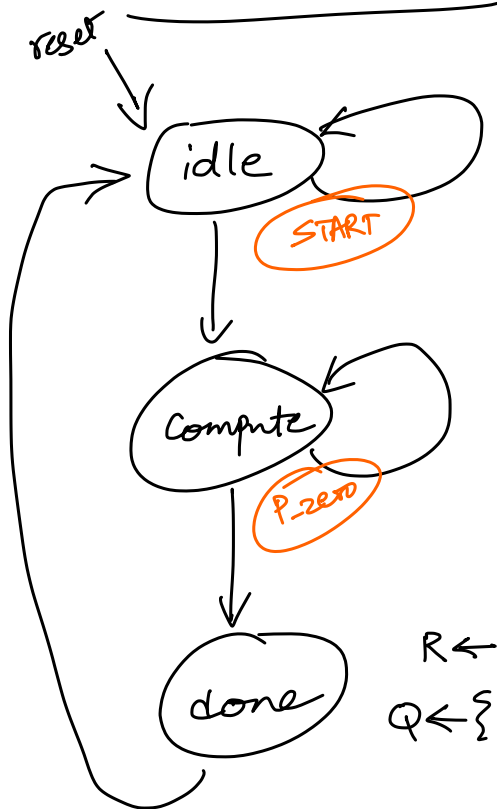

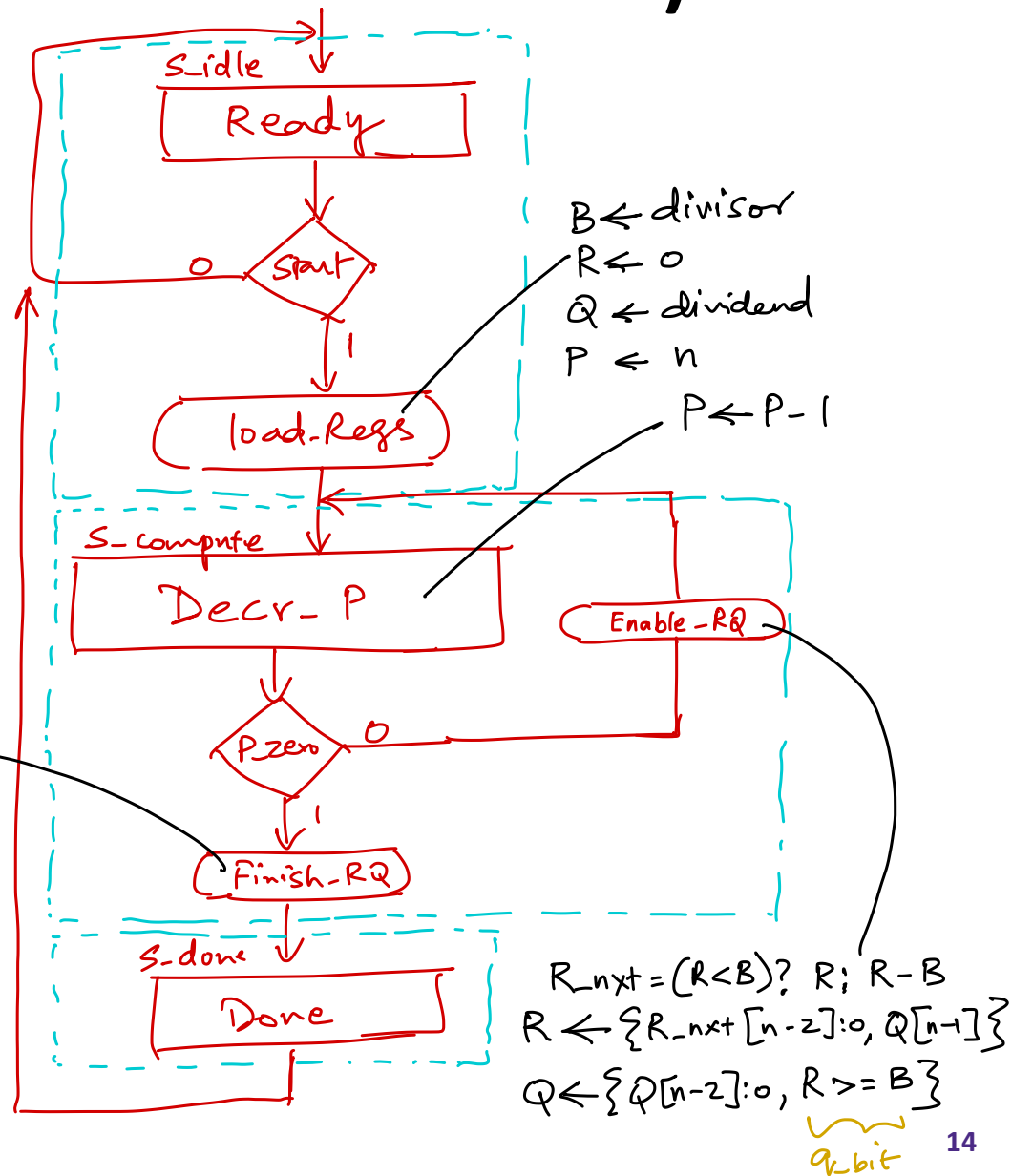$R \leftarrow (R < B) ? R : R - B$
 $Q \leftarrow \{Q[n-2]:0, R \geq B\}$
 (underlined $Q[n-2]$ is labeled q_bit)



Division Circuit Implementation

❖ Controller Logic

$$\text{Load_regs} = S_idle \cdot \text{Start}$$

$$\text{Enable_RQ} = S_compute \cdot \overline{P_zero}$$

$$\text{Finish_RQ} = S_compute \cdot P_zero$$

$$\text{Decr_P} = S_compute$$

$$\text{Ready} = S_idle$$

$$\text{Done} = S_done$$

Division Circuit (SV, Datapath)

```
module datapath #(parameter WIDTH=4)
    (Q, P, divisor, dividend, clk,
     Load_regs, Enable_RQ, Enable_R, Decr_P);

    // port definitions
    output logic [2*WIDTH-1:0] product;
    output logic [WIDTH-1:0] Q, P; // note: unnecessary bits for P
    input  logic [WIDTH-1:0] multiplicand, multiplier;
    input  logic clk, Load_regs, Shift_regs, Add_regs, Decr_P;

    // internal logic
    logic [WIDTH-1:0] B, R, R_tmp, R_nxt;
    logic q_bit;

endmodule
```

Division Circuit (SV, Datapath)

```
module datapath #(parameter WIDTH=4)
    (Q, P, divisor, dividend, clk,
     Load_regs, Enable_RQ, Enable_R, Decr_P);

    // port definitions & internal logic
    ...

    // assignments
    assign q_bit = (R >= B);
    assign R_tmp = (R < B) ? R : R-B;
    assign R_nxt = {R_tmp[WIDTH-2:0], Q[WIDTH-1]};
    assign Q_nxt = {Q[WIDTH-2:0], q_bit};

    // datapath logic
    always_ff @(posedge clk) begin
        if (Load_regs) begin
            R <= 0;      Q <= dividend;
            P <= WIDTH;  B <= divisor;
        end
        if (Decr_P)      P <= P - 1;
        if (Comp_regs)   {R, Q} <= {R_nxt, Q_nxt};
        if (Done_regs)   {R, Q} <= {R_tmp, Q_nxt};
    end // always_ff

endmodule
```

Lab 4 Preview: Bit Counter

- ❖ Design a circuit that counts the number of bits in a register *A* that have the value 1
- ❖ Algorithm:

```
B = 0;    // counter
while A != 0 do
    if A[0] = 1 then
        B = B + 1
    endif
    A = A >> 1
endwhile
```

EE/CSE 371

Design of Digital Circuits and Systems


Lecture 9: Algorithms to Hardware II

Arithmetic
mean

X

Sorting

Arithmetic Mean

 

- ❖ Design a sequential circuit that computes the mean M of k n -bit numbers stored in registers

- e.g., accessing a RAM or register file with k addresses
 - To save on hardware, you can only use one n -bit adder and have a single read port RAM

- ❖ Algorithm Pseudocode:

① $S = 0$
 for $i = 0$ to $k-1$
 $S = S + R[i]$
 end for
 $M = S/k$

② $S = 0$
 for $i = (k-1)$ to 0
 $S = S + R[i]$
 end for
 $M = S/k$

③ $M = 0$
 for $i = k-1$ to 0
 $M = M + R[i]/k$
 end for

Aside: Counter Variable

equality
detectors ✓


XNOR

- ❖ Many sequential hardware algorithms utilize counters
- ❖ If both work, is there a preference?

- How to implement $C = k - 1$ check?

$$C = C_{n-1} C_{n-2} \dots C_1 C_0$$
 
$$K-1 = (K-1)_{n-1} (K-1)_{n-2} \dots (K-1)_1 (K-1)_0$$





$$[C - (K-1)] \stackrel{?}{=} 0$$

- How to implement $C = 0$ check?



Better

  

Arithmetic Mean Specification

❖ Datapath

- A k -address *register file* (only using `r_addr` and `r_data`)
- Reg file address stored in $\lceil \log_2(k) \rceil$ *down-counter* A
- Sum stored in register S
- An n -bit *divider* circuit, as discussed last lecture

❖ Control

- Inputs *Start* and *Reset*, outputs *Ready* and *Done* ✓ ✓ *status indicators.*
- Status signals: *A_zero* , *Div_done (?)*
- Control signals: *Load-regs* , *Add* , *Divide* , *Decr-A* .