

Design of Digital Circuits and Systems, Lab 3

Digital Signal Processing

Lab Objectives

In this lab, you will use the audio coder/decoder (CODEC) on the DE1-SoC board to generate and filter noise from both an external source and an internal memory.



Using audio with the DE1-SoC via LabsLand involves some special instructions so make sure to reference the *Audio_Guide.pdf* document before you do any testing on the hardware!

Introduction

Sounds, such as speech and music, are signals that change over time. The amplitude of a signal determines the volume at which we hear it. The way the signal changes over time determines the type of sounds we hear. For example, an “ah” sound is represented by a waveform shown in Figure 1. The waveform is an *analog* signal, which can be stored in a *digital* form by using a relatively small number of samples that represent the analog values at certain points in time. The process of producing such digital signals is called **sampling**. The points in Figure 2 provide a sampled waveform. All points are spaced equally in time and they trace the original waveform.



Figure 1: An example waveform for an “ah” sound.

 


Figure 2: Sampled waveform of Figure 1.

The DE1-SoC board is equipped with an audio CODEC capable of sampling sound from a microphone and providing it as an input to a circuit. By default, the CODEC provides 48000 samples per second (48 kHz), which is sufficient to accurately represent audible sounds (by the Nyquist-Shannon sampling theorem).

To simplify this lab, a system that can record and play back sounds on the board is provided as a “starter kit.” The system comprises a Clock Generator, an Audio CODEC Interface, and an Audio/Video Configuration module (Figure 3). For this lab, we will assume that our audio will be split into two *channels*, left and right, that are intended to be played from multiple speakers (*e.g.*, left and right earbuds/headphones).

The left column of signals in Figure 3 are the inputs and outputs of the system. These I/O ports supply the clock inputs and connect the Audio CODEC and Audio/Video Configuration modules to the corresponding peripheral devices on the DE1-SoC board. The right column of signals connects the Audio CODEC Interface module to your circuit and allows your circuit to record sounds from a microphone and play them back via speakers.

 


Figure 3: The audio system used in Lab 3.

The system works as follows (this interface is also detailed in the starter kit files):

- Upon reset, the Audio/Video Configuration begins an auto-initialization sequence. The sequence sets up the audio device to sample microphone input at a rate of 48 kHz and produce output through the speakers at the same rate.
- Once the auto-initialization is complete, the Audio CODEC begins reading the data from the microphone once every 48,000-th of a second and sends it to the Audio CODEC Interface core in the system. **Note that this is significantly SLOWER than the DE1-SoC's onboard 50 MHz clocks.**
- Once received, a sample is stored in a 128-element buffer in the Audio CODEC Interface core. The first element of the buffer is always visible on the readdata_left and readdata_right outputs (i.e., 2 channels for 1 sample), but **the data is only valid when the read_ready signal is asserted**. When you assert the read signal, the current sample is replaced by the next element one or more clock cycles later, indicated by read_ready being reasserted.
- The procedure to output sound through the speakers is similar. Your circuit should **monitor the write_ready signal**. Only when the Audio CODEC is ready for a write operation should your circuit assert the write signal to write a sample from the writedata_left and writedata_right signals. This operation stores a sample in a buffer inside of the Audio CODEC Interface, which will then send the sample to the speakers at the right time.

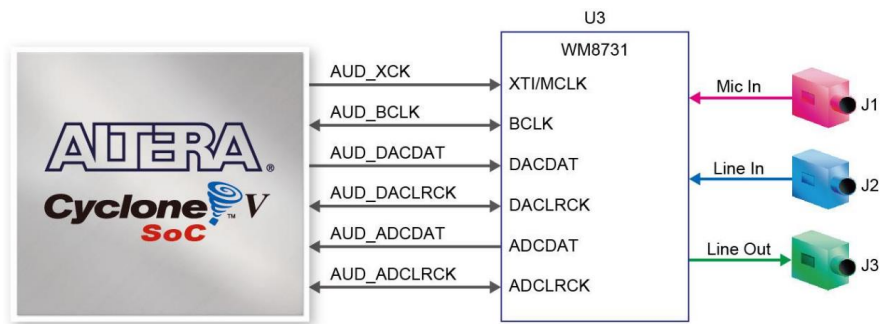


Figure 4: Connections between the FPGA and the Audio CODEC.

Task #1 – Passing Music Through the FPGA

In this task, you will play a music file into the audio input of the DE1-SoC, which will simultaneously be played through the audio output of the device.

- 1) Modify the provided starter kit circuit to pass the audio input to audio output *only when the CODEC is ready*. Hint: BOTH the audio input and audio output have to be ready for data passing!
- 2) In LabsLand, upload an audio file (either the provided *piano_noisy.mp3* or your own – see *Audio_Guide.pdf* for restrictions) alongside your synthesized circuit and verify that the preview of the audio file matches your recorded output sample. Recall that in LabsLand, you must record while playing the audio file into the DE1-SoC.



It is *critical* that you get the code for this task correct, as your understanding of the communication protocol with the audio CODEC will affect your ability to do the rest of the lab correctly. Once you have completed this task, you can post privately on Ed Discussion or drop by an office hour and a staff member will be happy to verify your setting of the read and write signals.

Task #2 – Play a Tone from Memory

In this task, you will produce a static tone from memory. By storing the samples from a sound's waveform, you can play back those samples later to re-produce the sound. We have provided a Python script which generates MIF files for a desired tone, which can then be loaded into memory. Information on how to use this Python script can be found in the tutorial document *note_gen_tutorial.pdf*.

- 1) Follow the tutorial on using the python script to create a MIF file with your desired tone. Create a ROM that initializes to the values stored in the MIF file using Quartus' built in library modules:
 - a. Open the IP Catalog in the Quartus menu by clicking on Tools → "IP Catalog". In the IP Catalog window, expand "Library", then "Basic Functions", then "On Chip Memory". Then double-click "**ROM: 1-PORT**".
 - b. Give the file an appropriate name, select "Verilog" as the file type, then click "OK" to open the configuration wizard.
 - c. In the first window specify 24-bits as the word width. You will need to check your generated MIF file to find the number of words, as this will vary. select "M10K" for memory block type and "Single clock" for the clocking method, then click "Next >".
 - d. Click "Next >" past the "Regs/Clocken/Aclrs" window keeping the default selections.
 - e. In the next window, under "Do you want to specify the initial contents of memory?", select "Yes, use this file for the memory content data" and specify your MIF file. Click "Finish" to use the rest of the default settings, then click "Finish" again at the summary page to exit the wizard. If prompted, add the new Quartus Prime IP File to your project by clicking "Yes".
- 2) Output the values stored in your ROM sequentially to the Audio CODEC, looping back to the start when you reach the end. Make sure to increment the address only once each time you write.
- 3) Compile and download your overall design to the DE1-SoC board, record the generated tone in LabsLand and then listen to the generated tone played from the FPGA.

- 4) Combine your Task #1 and Task #2 by instantiating them in a single top-level module that plays the input audio (Task #1) when SW9=0 and your tone from memory (Task #2) when SW9=1. While testing, you should switch between the tasks about halfway through your recording.

Task #3 – FIR Filter Size

In this task, you will learn a basic signal processing technique known as **filtering**. Filtering is a process of adjusting a signal (*e.g.*, removing noise). **Noise** in a sound waveform is represented by small, but frequent changes to the amplitude of the signal.

A simple logic circuit that achieves the task of noise-filtering is an averaging **Finite Impulse Response (FIR)** filter. An averaging filter removes noise from a sound by averaging the values of adjacent samples. Conceptually, a basic FIR filter uses registers as delay blocks and computes the moving average from their outputs, as shown in Figure 5.

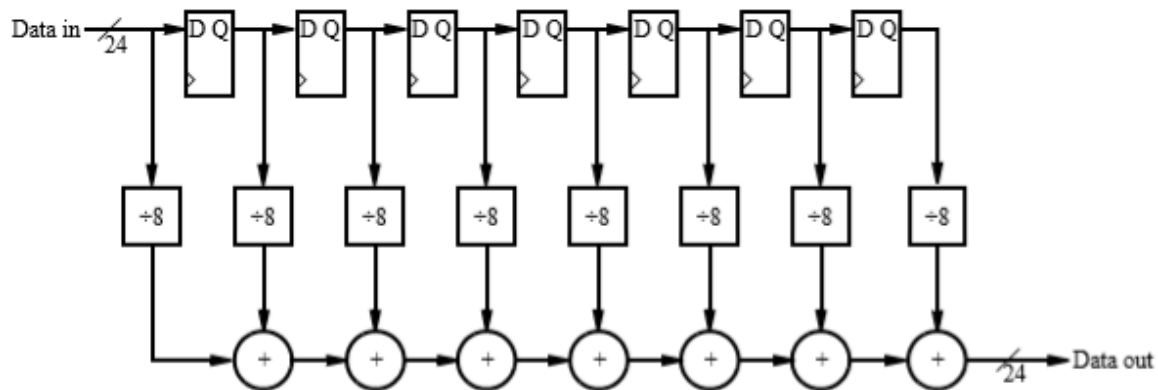


Figure 5: A Finite Impulse Response (FIR) filter that takes a moving average of 8 samples. While this is conceptually what we want to achieve in Task #3, we will use a different implementation, as shown in Figure 6.

However, we can achieve the same result using a FIFO buffer and accumulator (*i.e.*, a register whose input is the sum of the next incoming data value and its current stored value), as shown in Figure 6.

 


Figure 6: N -sample averaging FIR filter using a FIFO buffer and accumulator that you will implement in Task #3.

To compute the average of the last N samples, this circuit first divides the input sample by N . Then, the resulting value is stored in a First-In First-Out (FIFO) buffer of length N and added to the accumulator. To make sure the value in the accumulator is the average of the last N samples, the circuit subtracts the value that comes out of the FIFO, which represents the $(N + 1)^{\text{th}}$ sample.



Arithmetic can cause strange behaviors when synthesized onto your board, particularly because wire and logic are, by default, unsigned data types but we are using them for signed arithmetic:

- The most robust way to divide by a power of two is using an arithmetic right shift. The following code snippet uses the replication and concatenation operators to divide the w -bit signal data by 2^n : `assign divided = {{n{data[w-1]}}}, data[w-1:n]};`
- Please pay attention to Figure 6 and make sure that you adding data_out multiplied by -1 instead of subtracting.



Task #3 is by far the most difficult part of this lab. Here are some tips to help you out:

- Although the starter kit includes an Altera library FIFO buffer, we recommend using the circular queue implementation from lecture and hw3 for familiarity and ease of use.
- Carefully consider how to ensure that your FIR filter updates when it is supposed to. As a single system, the FIFO buffer and accumulator should be synchronized together (*i.e.*, at any clock trigger, either both or neither should update). But when should they update based on the CODEC signals?
- The description below Figure 6 is accurate once the FIFO buffer is full. However, you should carefully consider what your buffer will do while the first $N-1$ samples are read (*i.e.*, at the beginning or after a reset) and make sure that the value of the accumulator also matches the buffer behavior during this time period.

- 1) Implement the N -sample averaging FIR filter. Use SW8 to select between filtered (SW8=1) and unfiltered (SW8=0) audio to output; this filtering should be able to interact with *both* Task #1 (SW9=0) and Task #2 (SW9=1).
- 2) Compile and download your overall design to a DE1-SoC board in LabsLand and use *piano_noisy.mp3* to generate your recorded output.
- 3) **Experiment with different values of N to see what happens to the noisy audio sample.** Use the switch to tell what kind of effect the filter is having on the audio.
 - a) When you change N , remember to adjust *both* the FIFO buffer length and the circuit divisor. We recommend experimenting with values of N that are powers of 2 for easier division.

Lab Demonstration/Turn-In Requirements

In-Person Demo

- Demonstrate all working Tasks using SW9 and SW8, with your FIR filter size N set to the “best” length that you found. You will need *piano_noisy.mp3* uploaded.
- Briefly walk your TA through your N -sample averaging FIR filter SystemVerilog file.
- Be prepared to answer 1-2 questions about your lab experience to the TA.

Lab Report (submit as PDF on Gradescope)

- Include the required **Design Procedure**, **Results**, and **Experience Report** sections.
 - You only need to include simulations for modules you have written, you can assume all of the provided files work without simulation.
 - Task #1: The design can be a short description and/or a small circuit diagram. No simulation needed.
 - You should omit top-level simulations for this lab, as mimicking the AUD and I2C signals is unreasonable. However, you should still include a top-level block diagram and description. Do *not* just include Figure 3 – we need to see/know what happens in “Your Circuit”!
- Don’t forget to also submit your SystemVerilog files (.sv), including testbenches!

Lab 3 Rubric

Grading Criteria	Points
Name, student ID, lab number	2 pts
Design Procedure <ul style="list-style-type: none">▪ Do discuss Task #1, but explicit diagram may be unnecessary; include and discuss designs for ROM and FIR filter modules.▪ Top-level block diagram can build off of Figure 3 but should include connections between your defined modules.	14 pts
Results <ul style="list-style-type: none">▪ No simulations needed for provided/reused modules, Task #1, or top-level module	14 pts
Experience Report	6 pts
SystemVerilog code uploaded	5 pts
Code Style	5 pts
LAB DEMO	54 pts
	100 pts